

# Introduction to Operational Amplifiers

①

Syllabus: Ideal OPAMP, Inverting and Non-inverting OP-AMP circuits, OP-AMP applications: Voltage follower, addition, subtraction, integration, differentiation, Numerical examples as applicable.

## \* Operational amplifier or OP-amp:

An OP-amp is a very high gain differential amplifier with high input impedance and low output impedance.

①

An OP-amp is a direct-coupled high-gain amplifier usually consisting of one or more differential amplifiers and usually followed by a level translator and an output stage.

### Note:

- ① An OP-amp is a linear integrated circuit (IC)
- ② The OP-amp is a versatile device (used to amplify both AC and DC input signals)
- ③ OP-amp is used to perform mathematical operations such as addition, subtraction, differentiation and integration.
- ④ Robert J. Widlar invented  $\mu A 741$  IC (An internally compensated OP-amp) in 1968.

MA  $\rightarrow$  Fairchild (Manufacturer)

- ⑤ Advantages of OP-AMP over transistor amplifier
  - Less power consumption
  - Low cost
  - More compact
  - More reliable
  - Easy design
  - Versatile device
  - Higher gain can be obtained etc

## ⑥ Applications of OP-amp

- AC and dc signal amplification
- Active filter.
- Oscillator
- Comparator
- Regulator
- Biomedical instrumentation. etc

④ Pin diagram of OP-amp (741 IC)

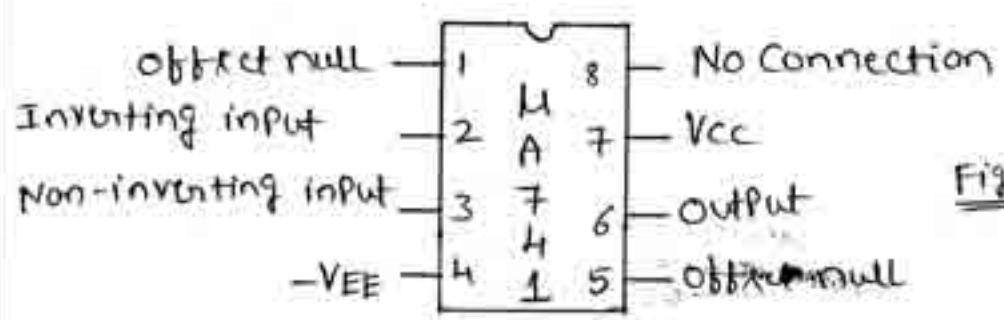


Fig ④: Pin diagram of op-amp

⑤ Circuit Symbol of OP-amp ⑥ Schematic Symbol

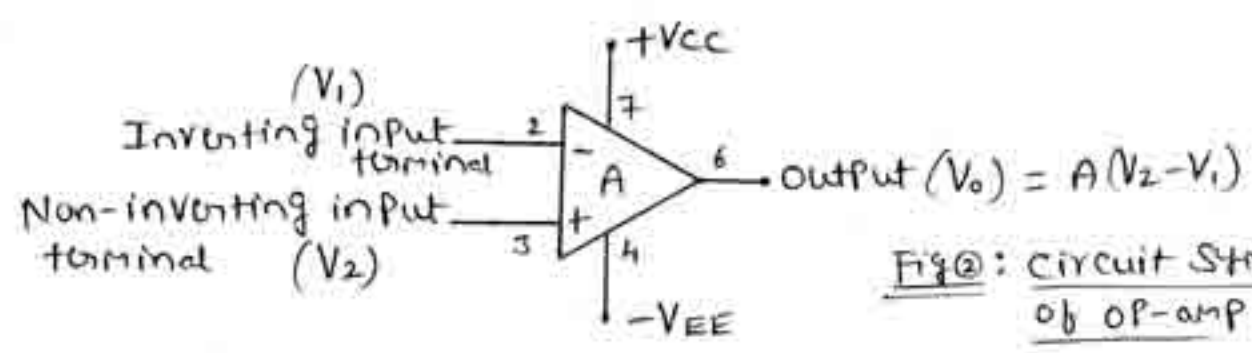


Fig ⑤: Circuit Symbol of op-amp

⑦ Single-Ended Input: Input signal is connected to one input with the other input connected to ground.

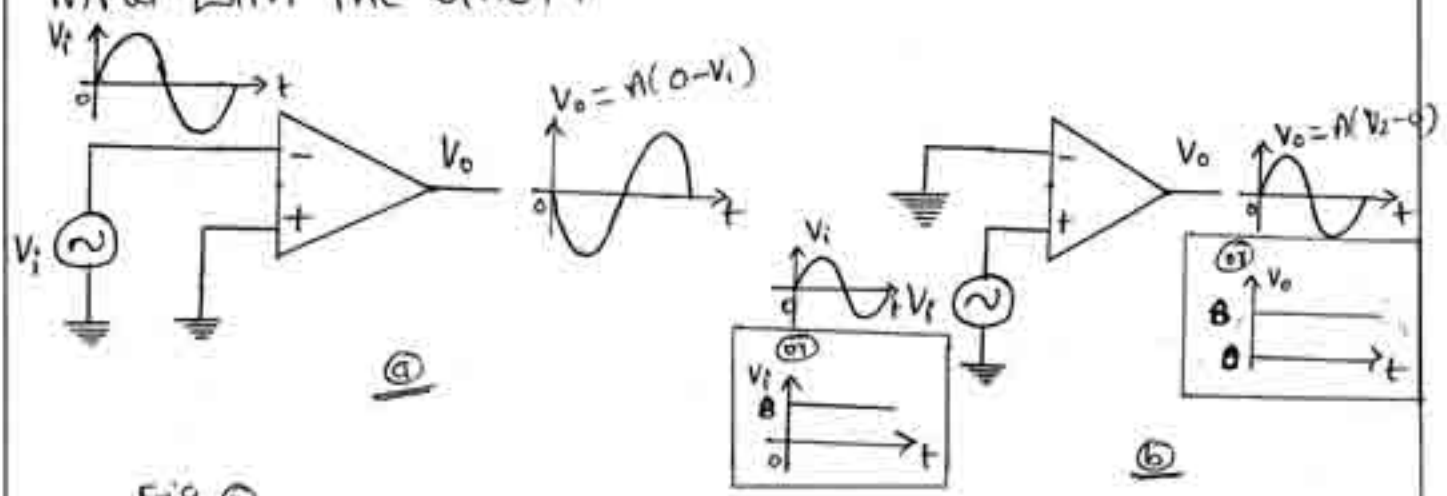


Fig ⑥

### ⑩ Double-Ended (Differential) Input :

Input signals are applied to each input

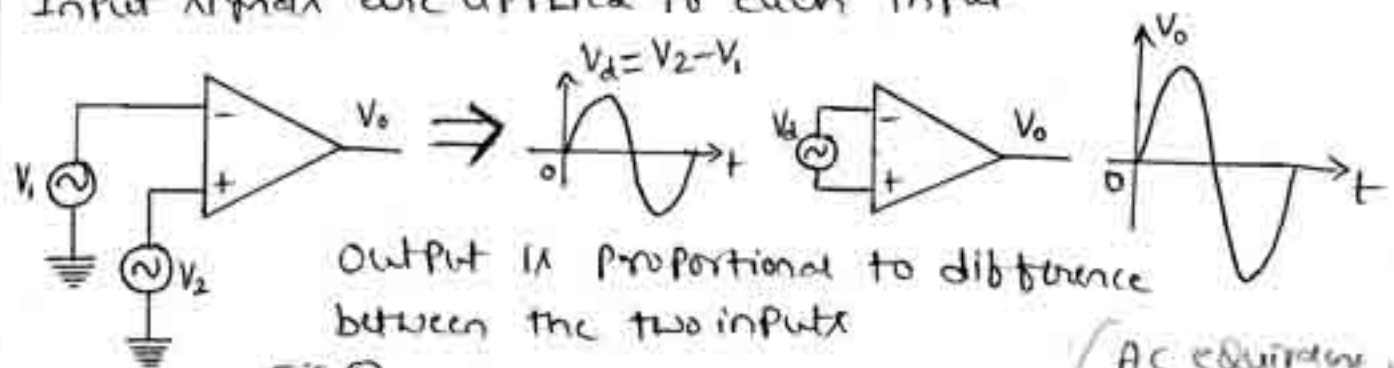


Fig 4

(AC equivalent circuit)

### ⑪ Equivalent circuit @ Circuit model of op-amp : ckt

Fig 5 shows the simplified circuit model of Practical op-amp.

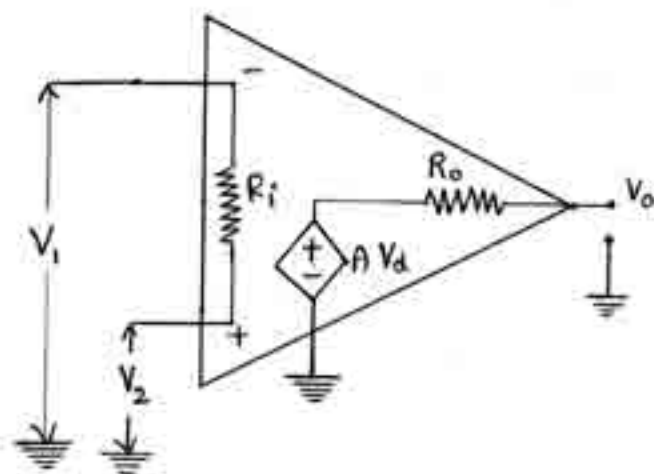


Fig 5 : circuit model of Practical op-amp

→  $AV_d [A(V_2 - V_1)]$  is the Thevenin equivalent Voltage source, &  $R_o$  is the Thevenin equivalent resistance

→  $A$  is the gain @ Large signal Voltage gain

→  $R_i$  is the input resistance

→  $V_d (V_2 - V_1)$  is the difference input Voltage.

Fig 6 shows the Equivalent circuit of ideal op-amp.

→ An ideal op-amp has  
 $A = \infty$ ,  $R_i = \infty$ , &  $R_o = 0$

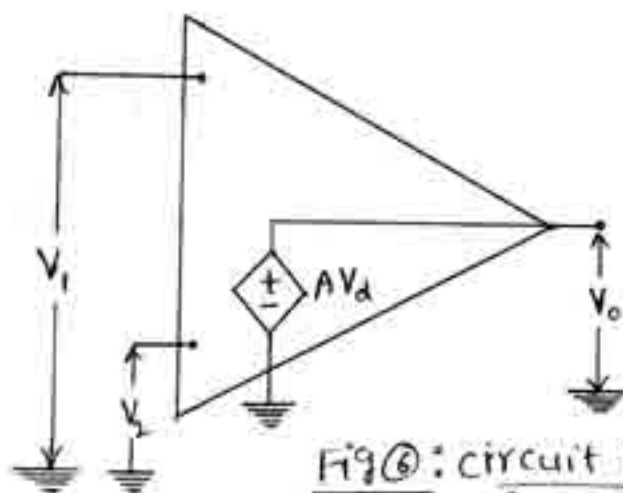


Fig 6 : circuit model of ideal op-amp

# 11) Package types

There are three basic types of Linear IC Packages:

- Ⓐ The Flat Pack
- Ⓑ The Metal Can
- Ⓒ Transistor Pack
- Ⓓ The dual-in-line Package (DIP)

# 12) Features of 741

- No external frequency compensation required
- Short-circuit Protection.
- Offset null capability
- Large common-mode and differential voltage range.
- Low power consumption.
- No Latch-up Problem.

# 13) Differential amplifier:

It amplifies the difference of the two inputs  $V_d (V_2 - V_1)$

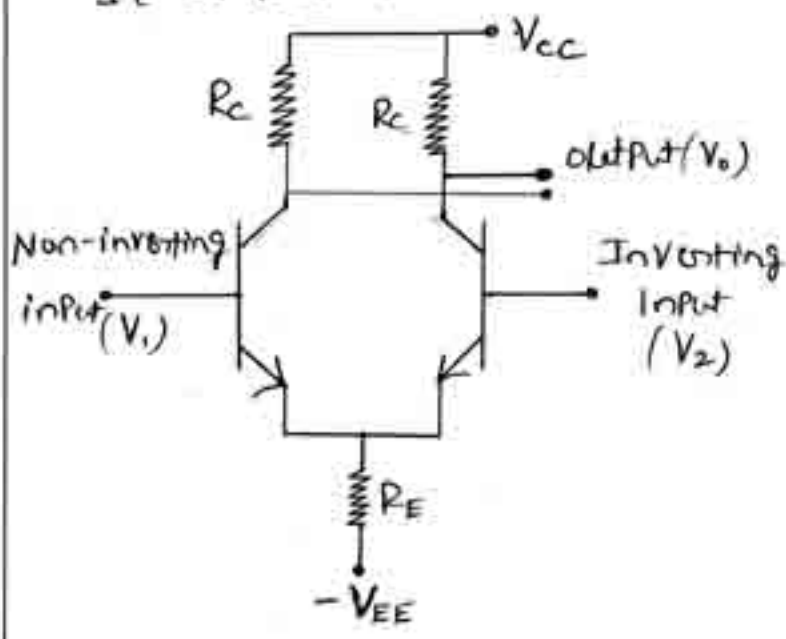


Fig ⑦: Differential amplifier

Output is,

$$V_o \propto (V_1 - V_2)$$
$$\Rightarrow V_o = A(V_1 - V_2) \quad \text{⑧}$$
$$V_o = A V_d$$

- Where,
- $A \rightarrow$  Large signal Voltage gain
  - $V_1 \rightarrow$  Voltage applied to the non-inverting input
  - $V_2 \rightarrow$  Voltage applied to inverting input
  - $V_d \rightarrow$  Difference voltage

- Ⓐ OP-amp which use BJT are called bipolar type opamp
- OP-amp having FET input circuit with the remainder of the circuit using BJT are called FET type OP-amp

\* Block diagram of OP-amp @ Internal Block diagram

① Architecture of op-amp:

The block diagram of an OP-amp is shown in fig ⑧

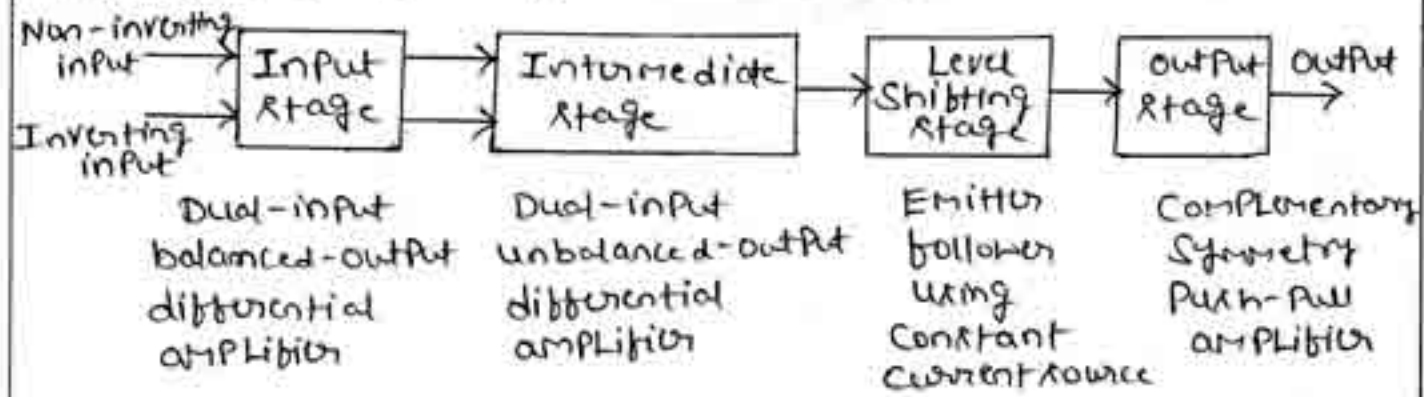


Fig ⑧: Block diagram of a typical OP-amp

There are four stages:

- ① Input stage @ Differential amplifier stage
  - It can amplify difference between the two input signals.
  - Input resistance is very high, draws zero current from the input sources.
- ② Intermediate stage (stage) @ High gain amplifier stage
  - It uses direct coupling.
  - It provides very high gain.
- ③ Level translator stage @ Level Shifter stage (Buffer)
  - It shifts the dc level of the output voltage of the intermediate stage to zero.
- ④ Output stage @ Power amplifier stage @ driver stage
  - It has very small output resistance.
  - output voltage is the same irrespective of the value of the load resistance connected to the output terminal.

Note: ① Configurations @ Voltage gain of OP-amp:



## ① Open-loop Configuration @ Open-loop Voltage gain ( $A_{OL}$ )

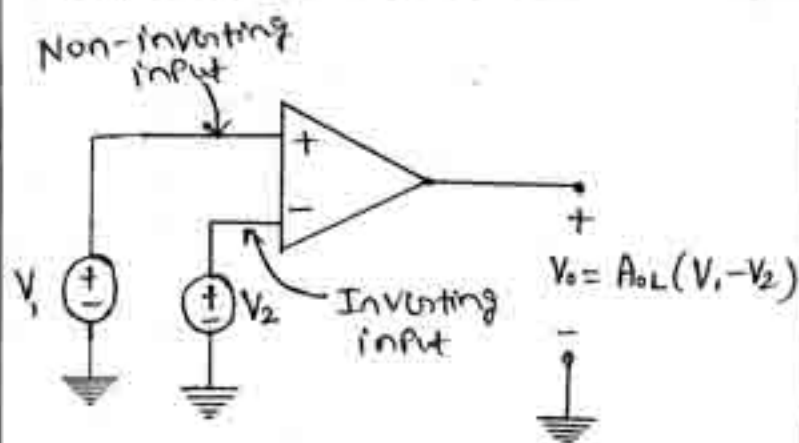


Fig ①: Open Loop Configuration

- $A_{OL}$  is the open-loop voltage gain of op-amp (Typically  $A_{OL} = 2 \times 10^5$ )
- $A_{OL}$  is the maximum possible voltage gain.
- There is no feedback from the output to input

- If input is in micro Volts, output will be in Volts.
- Output voltage cannot cross the value of power supply (or saturation value)  $V_{CC}$  (or  $V_{EE}$ )
- So, if input is in milli Volts, output reaches saturation value  $V_{sat} = V_{CC}$  (or  $V_{EE}$ ). This property of op-amp is called Saturation Property.

## ② Closed-loop Configuration @ Closed-loop Voltage gain ( $A_{CL}$ )

- Open-loop voltage gain of op-amp is very high. Such high gain is not required in most applications.
- In order to reduce gain, negative feedback is used (a part of the output signal is fed back in phase opposition to the input)

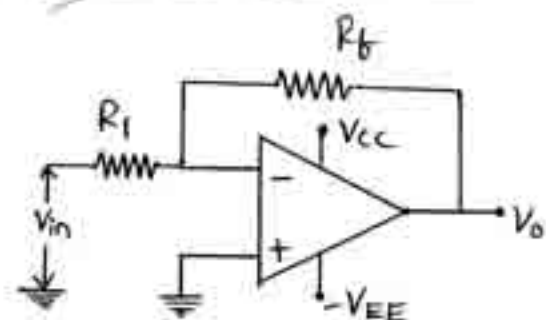


Fig ②: Negative feedback op-amp circuit (Closed loop configuration)

- Many other op-amp characteristics are improved with this.

## ③ Total output of a differential amplifier (practically) @ (op-amp)

The output of OP-amp (DA) is. (DA  $\rightarrow$  Differential Amplifier)

$$V_o = A_d V_d \quad \text{--- (1)}$$

Where,  $A_d \rightarrow$  Differential gain (Gain with which the DA amplifies the difference between two input signals)

$V_d \rightarrow$  Difference between two inputs ( $V_1 - V_2$ )

$$A_d = \frac{V_o}{V_d}$$

If  $V_1 = V_2$ , then ideally output is zero ( $V_o = 0$ )

But in practical OP-amp, output is.

$$V_o = A_{cm} V_{cm} \quad \text{--- (2)}$$

$$A_{cm} = \frac{V_o}{V_{cm}}$$

Where  $A_{cm} \rightarrow$  common mode gain (Gain with which DA amplifies the common mode signal)

$V_{cm} \rightarrow$  Common mode signal ( $\frac{V_1 + V_2}{2}$ )

$\therefore$  Total output is.

$$V_o = A_d V_d + A_{cm} V_{cm}$$

$$V_o = A_d V_d \left( 1 + \frac{1}{CMRR} \frac{V_{cm}}{V_d} \right) \quad \left[ \because CMRR = \frac{A_d}{A_{cm}} \right]$$

$$\textcircled{III} A_d (\text{dB}) = 20 \log_{10}(A_d)$$

OP-amp parameters @ Characteristics (Large signal voltage gain) (A)

① Differential gain @ Differential mode gain ( $A_d$ )

It is the factor by which the difference between the two input signals is amplified by the OP-amp.

②

It is the ratio of the output voltage to the difference voltage. It is denoted by  $A_d$ .

ie  $A_d = \frac{V_o}{V_d} = \frac{V_o}{V_1 - V_2}$

Ideally:  $A_d = \infty$   
Practically:  $A_d = A = 2 \times 10^5$   
(HA741)

② Common Mode gain ( $A_{cm}$ )

It is the factor by which the common mode input voltage is amplified by the OP-amp.

It is the ratio of the output voltage to the common mode signal. It is denoted by ' $A_{cm}$ '

ie  $A_{cm} = \frac{V_o}{V_{cm}} = \frac{V_o}{(V_1 + V_2)/2}$

Ideally:  $A_{cm} = 0$   
Practically:  $A_{cm} = 6-7$   
(HA741)

③ Common Mode rejection ratio (CMRR)

It is the factor which explains the ability of an OP-amp to reject the common mode signal.

It is the ratio of differential gain to common mode gain. It is denoted by 'CMRR'.

ie  $CMRR = \frac{A_d}{A_{cm}}$       ①  $CMRR(dB) = 20 \log_{10} \left( \frac{A_d}{A_{cm}} \right) (dB)$

Ideally:  $CMRR = \infty$   
Practically:  $CMRR = 90dB$   
(HA741)

( $A_d$  is known as large-signal volt-sec gain A)

④ Differential input resistance ② Input resistance ③

Input impedance ( $R_i$ )

It is the equivalent resistance measured at either the inverting ② non-inverting input terminal with the other terminal connected to ground. It is denoted by ' $R_i$ '

Ideally:  $R_i = \infty$   
Practically:  $R_i = 2M\Omega$  (For HA741)

⑤ Output resistance ④ Output impedance ( $R_o$ )



It is the equivalent resistance measured between the output terminal of the OP-amp and the ground. It is denoted by  $R_o$ .

Ideally:  $R_o = 0$   
Practically:  $R_o = 75 \Omega$  (741C)

### ⑥ Bandwidth (BW)

It is the range of frequency over which the gain of OP-amp is almost constant.

It is the range of frequency over which the performance of the OP-amp is satisfactory. It is denoted by BW.

Ideally:  $BW = \infty$   
Practically:  $BW = 1 \text{ MHz}$  (741C)

741C IC is  
Range of 741C

### ⑦ Input offset voltage ( $V_{io}$ )

It is the voltage that must be applied between the two input terminals of an OP-amp to make output voltage zero (to null the output). It is denoted by  $V_{io}$ .

Ideally:  $V_{io} = 0$   
Practically:  $V_{io} = 6 \text{ mV}$  (741C)

$V_{io} = V_1 - V_2$  for  
 $V_o = 0$

### ⑧ Output offset voltage ( $V_{oo}$ )

It is the output voltage when both input voltages are zero. It is denoted by  $V_{oo}$ .

Ideally:  $V_{oo} = 0$   
Practically:  $V_{oo} = 1 \text{ mV}$  (741C)

### ⑨ Input offset current ( $I_{io}$ )

It is the difference between the currents in the input terminals. It is denoted by  $I_{io}$ .

$$\text{i.e. } I_{io} = |I_1 - I_2|$$

Where,  $I_1 \rightarrow$  current into the noninverting input

$I_2 \rightarrow$  current into the inverting input.

Ideally:  $I_{io} = 0$

Practically:  $I_{io} = 20 \text{ nA}$  (For  $\mu\text{A} 741$ )

20 nA max

### ⑩ Input bias current ( $I_{ib}$ )

It is the average of the currents in the input terminals. It is denoted by  $I_{ib}$ .

$$\text{i.e. } I_{ib} = \frac{I_1 + I_2}{2}$$

Where,  $I_1, I_2 \rightarrow$  current into non-inverting & inverting input respectively.

Ideally:  $I_{ib} = 0$

Practically:  $I_{ib} = 80 \text{ nA}$  (For  $\mu\text{A} 741$ )

80 nA max

### ⑪ Slew rate (SR)

It is the maximum rate of change of output voltage with respect to time. It is denoted by SR.

$$\text{i.e. } SR = \left. \frac{dV_o}{dt} \right|_{\text{max}} \quad (\text{V}/\mu\text{s})$$

Ideally:  $SR = \infty$

Practically:  $SR = 0.5 \text{ V}/\mu\text{s}$

### ⑫ Supply voltage rejection ratio ① Power supply sensitivity ② Power supply rejection ratio ③: $(SVRR)$ ④ $(PSRR)$

It is the change in input offset voltage ( $V_{io}$ ); caused by variations in supply voltage. It is denoted

by SVRR @ PSRR.

$$\text{ic } SVRR = \frac{\Delta V_{io}}{\Delta V} (\mu V/V)$$

Ideally:  $SVRR = 0$

Practically:  $SVRR = 150 \mu V/V$  (741C)

Note:

① Input Capacitance ( $C_i$ ):

It is the equivalent capacitance measured at either the inverting @ noninverting terminal with the other terminal connected to ground. It is defined by ' $C_i$ '.

Practically:  $C_i = 1.4 \text{ pF}$  for 741C

② Gain-Bandwidth product (GB)

It is the bandwidth of the OP-amp when the voltage gain is 1

Practically:  $GB = 1 \text{ MHz}$  for 741C

③ Maximum signal frequency interval of Slew rate (for an undistorted output)

Let the output Voltage (Sinusoidal signal) be.

$$V_o = V_m \sin(\omega t) \quad \text{--- ①}$$

Diff w.r.t 't' on both

$$\frac{dV_o}{dt} = V_m \cos(\omega t) \cdot \omega$$

$$\Rightarrow \left. \frac{dV_o}{dt} \right|_{\max} = \omega V_m \quad \text{--- ②} \quad (\because \cos(\omega t)|_{\max} = 1)$$

To prevent distortion at the output, the rate of change of output w.r.t must be less than the SR.

$$\text{i.e. } \left. \frac{dV_o}{dt} \right|_{\max} \leq SR \quad \text{--- (3)}$$

Using (2) in (3), we get,

$$\omega V_m \leq SR$$

$$\Rightarrow \omega \leq \frac{SR}{V_m} \Rightarrow \omega_{\max} = \frac{SR}{V_m} \quad (\text{rad/s})$$

$$\Rightarrow f \leq \frac{SR}{2\pi V_m} \quad (\because \omega = 2\pi f) \Rightarrow f_{\max} = \frac{SR}{2\pi V_m} \quad (\text{Hz})$$

#### ④ OP-amp characteristics:

Sl. No.	Parameter	Symbol	Ideal Value	Typical Value for 741
1	Differential gain @ Large signal Voltage gain @ Open-loop Voltage gain.	$A_d$ @ $A$	$\infty$	$2 \times 10^5$
2	Common mode gain	$A_{cm}$	0	6
3	Common mode rejection ratio	CMRR	$\infty$	90dB
4	Input resistance	$R_i$	$\infty$	2M $\Omega$
5	Output resistance	$R_o$	0	75 $\Omega$
6	Bandwidth	BW	$\infty$	1MHz
7	Input offset voltage	$V_{io}$	0	6mV
8	Output offset voltage	$V_{oo}$	0	1mV
9	Input offset current	$I_{io}$	0	20nA
10	Input bias current	$I_{ib}$	0	80nA
11	Slew rate	SR	$\infty$	0.5V/ $\mu$ s
12	Supply Voltage rejection ratio	SVRR	0	150 $\mu$ V/V

#### ⑤ Virtual ground @ Virtual short :

The OP-amp inverting amplifier is shown in fig (ii)

The output voltage is,

$$V_o = A(V_2 - V_1) \quad \text{--- (1)}$$

Where,  $A \rightarrow$  Large signal voltage gain

For an output voltage of 12V, the input voltage would be,

$$V_2 - V_1 = \frac{V_o}{A} \quad (\because \text{From 1})$$

$$\Rightarrow V_2 - V_1 = \frac{12}{2 \times 10^5} \quad (\because \text{Practically, } A = 2 \times 10^5 \text{ for } \mu A 741)$$

$$\Rightarrow V_2 - V_1 = 0.06 \text{ mV}$$


Differential input voltage is very small, ( $V_d = V_2 - V_1$ )

Ideally,  $V_2 - V_1 = 0$


$$\Rightarrow \boxed{V_1 = V_2} \quad \text{--- (2)}$$

From (2), we can conclude,

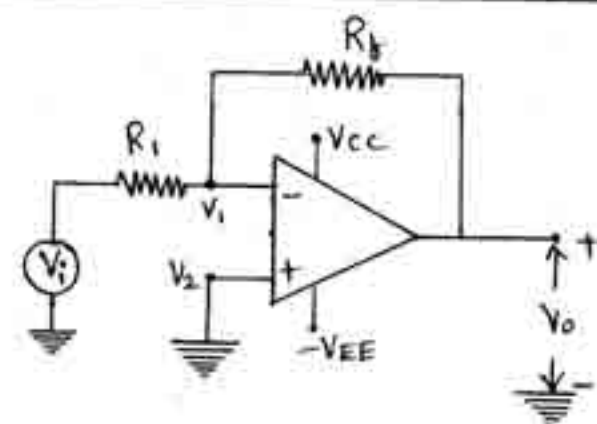- Voltage at inverting terminal = Voltage at non-inverting terminal
- There exists a virtual short-circuit @ virtual ground
- No current flows through the short circuit
- Current through  $R_i =$  Current through  $R_f$ .



Fig(11): Basic op-amp circuit

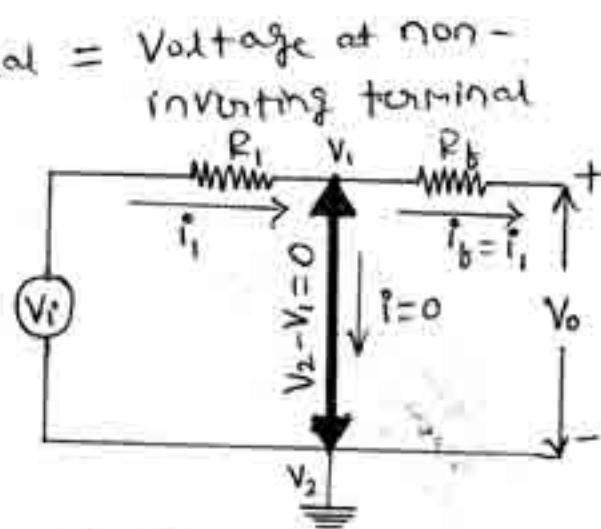

Fig(12): virtual ground

⑥ The virtual short is indicated by a thick line between input terminals.

⑦ For an op-amp, output voltage cannot cross  $V_{CC}(V_{EE})$  ( $\approx 12$  to  $15$  V) ( $\because$  From Saturation Property)



⑧ No current flows into OP-amp input terminals ( $\because$  Input impedance is Very high)


\* OP-amp APPLICATIONS

- |                           |   |
|---------------------------|---|
| ① Voltage follower        | ⑤ Subtractor (difference amplifier)     |
| ② Inverting amplifier     | ⑥ Differentiator                        |
| ③ Non-inverting amplifier | ⑦ Integrator                            |
| ④ Summer (Adder)          |   |
|                           | ⑧ Isolation amplifier ⑨ source follower |

\* ① Voltage follower ⑩ unity gain amplifier ⑪ buffer:

Definition: An OP-amp circuit in which the output voltage follows the input voltage is called Voltage follower (Output voltage is equal to input voltage)

Circuit diagram:

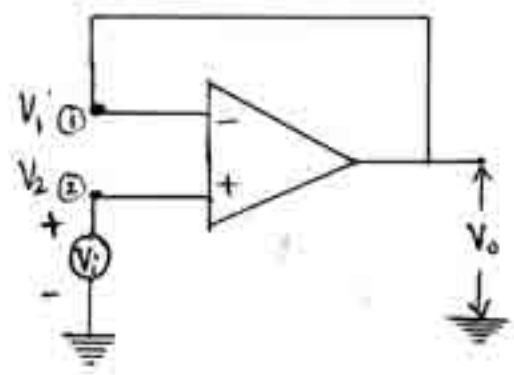

Analysis:

From Virtual ground concept,

$$V_1 = V_2 = V_i \quad \text{--- (1)}$$



Since output is connected to input,

$$V_o = V_i \quad \text{--- (2)}$$

From (1) & (2),

$$\boxed{V_o = V_i} \quad \text{--- (3)}$$

Wave form: DC

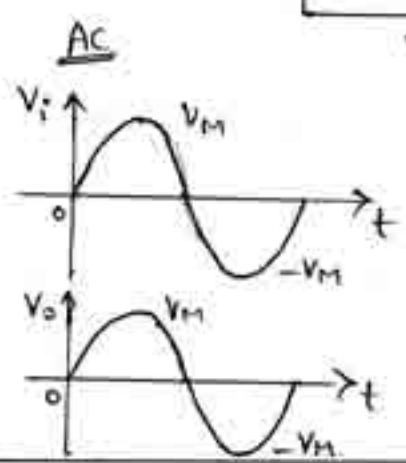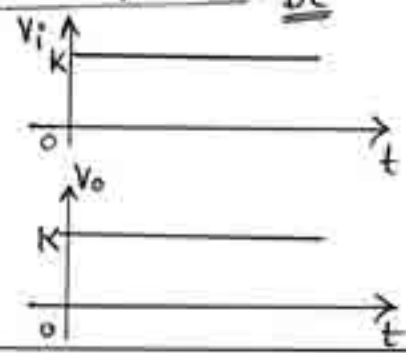



Conclusion:

- From eqn (3), the output voltage follows the input voltage


## \*② Inverting amplifier:

Definition: An OP-AMP circuit in which the output voltage is out of phase ( $180^\circ$ ) with respect to the input voltage is called inverting amplifier.

Circuit diagram:

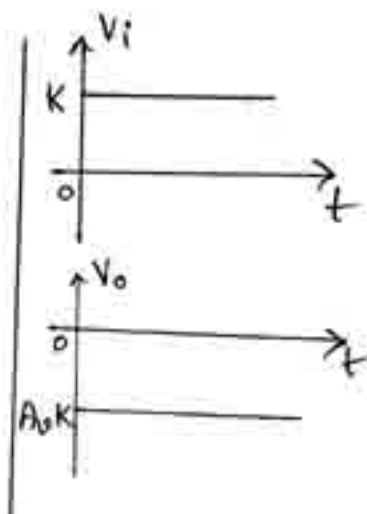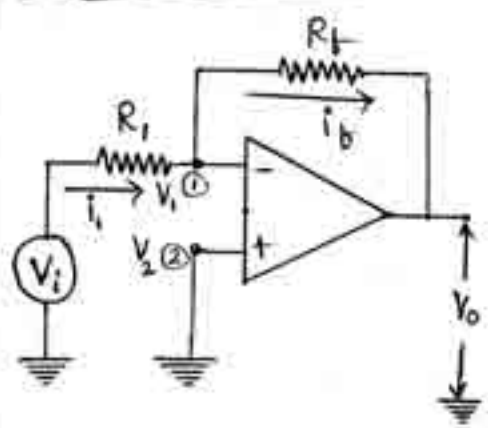

Waveform:

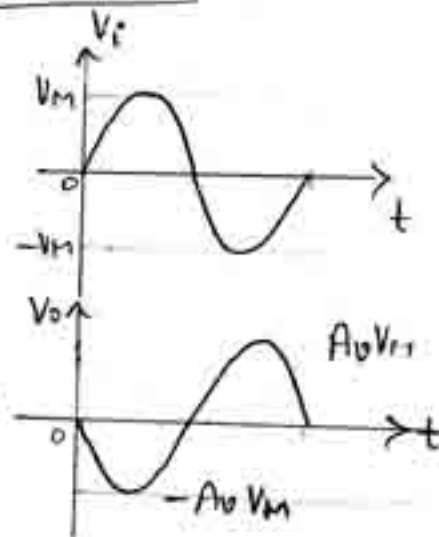

Analysis:

Applying KCL at node ①.

$$i_i = i_f \quad (\text{Since input impedance of OP-AMP is very high, no current flows into OP-AMP input terminals})$$

$$\Rightarrow \frac{V_i - V_1}{R_i} = \frac{V_1 - V_o}{R_f}$$

$$\Rightarrow \frac{V_i}{R_i} = -\frac{V_o}{R_f} \quad \left[ \begin{array}{l} \text{From Virtual Ground Concept,} \\ V_1 = V_2 = 0 \end{array} \right]$$

$$\Rightarrow \boxed{V_o = -\left(\frac{R_f}{R_i}\right)V_i} \quad \text{or} \quad \boxed{\frac{V_o}{V_i} = -\frac{R_f}{R_i} = A_v} \quad \text{--- (5)}$$

Where.


$A_v \rightarrow$  Closed loop Voltage gain

Conclusion: From eqn (5), negative sign indicates that the output is inverted w.r.t the input.


## \*③ Non-Inverting amplifier:

Definition: An op-amp circuit in which the output voltage is in phase with the input voltage is called Non-inverting amplifier.

Circuit diagram:

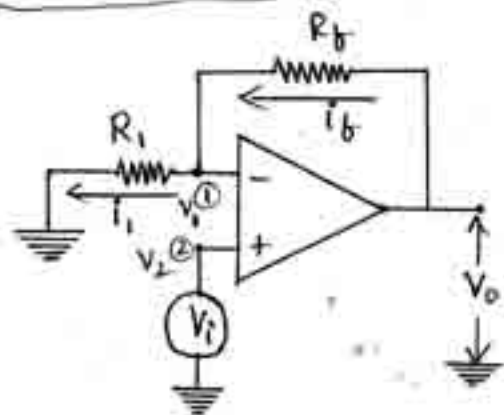

Waveform:

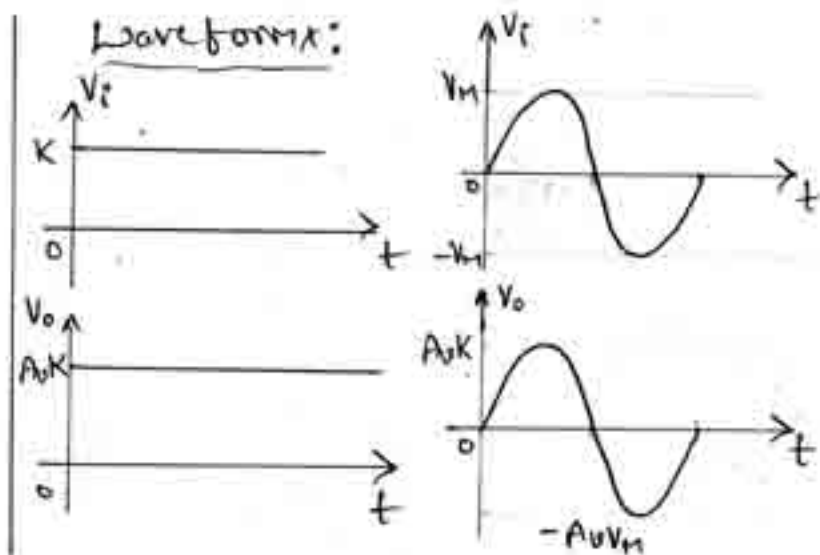

Analysis:

Applying KCL at node ①.

$$i_b = i_1 \quad \left( \because \text{No current flows into op-amp input terminals} \right)$$

$$\Rightarrow \frac{V_o - V_i}{R_f} = \frac{V_i - 0}{R_1} \quad \left( \text{From virtual ground concept, } V_1 = V_2 = V_i \right)$$

$$\Rightarrow \frac{V_o - V_i}{R_f} = \frac{V_i}{R_1}$$

$$\Rightarrow \frac{V_o - V_i}{V_i} = \frac{R_f}{R_1}$$

$$\Rightarrow \frac{V_o}{V_i} - 1 = \frac{R_f}{R_1}$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1} = A_v} \quad \text{--- ⑥} \quad \boxed{V_o = \left(1 + \frac{R_f}{R_1}\right) V_i} \quad \text{--- ⑦}$$

Where,  $A_v \rightarrow$  closed loop voltage gain.

Conclusion: From ⑥ & ⑦, • The output voltage is in-phase with the input voltage. •  $A_v$  depends on  $R_f$  &  $R_1$ .

## \* ⑥ Summer (adder) ⑦ Summing amplifier:


Definition: An op-amp circuit, in which the output voltage is the sum of the input signal voltages is called Summer.

There are ~~two~~ types:


### ① Inverting summing amplifier:

Definition: An op-amp circuit, in which the output voltage is the inverted sum of the input voltages is called inverting summing amplifier.

Circuit diagram

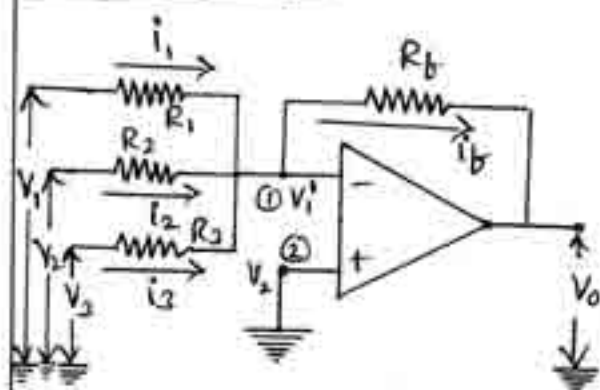

Waveform

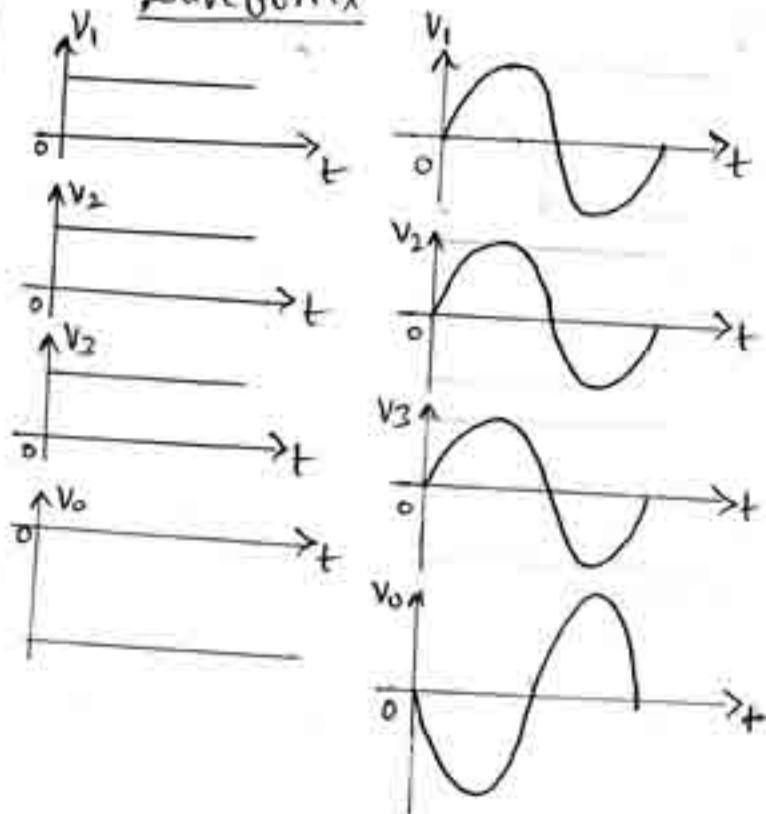

Analysis:

Applying KCL at node ①.

$$i_1 + i_2 + i_3 = i_f \quad (\because \text{No current flows into op-amp input terminals})$$

$$\Rightarrow \frac{V_1 - V_1'}{R_1} + \frac{V_2 - V_1'}{R_2} + \frac{V_3 - V_1'}{R_3} = \frac{V_1' - V_0}{R_f}$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_0}{R_f} \quad \left( \begin{array}{l} \text{From virtual ground concept,} \\ V_1' = V_2 = 0 \end{array} \right)$$

$$\Rightarrow \boxed{V_o = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)} \quad \text{--- (8)}$$

Conclusion:

From (8), the output voltage is proportional to the inverted sum of the input voltages.


Note:

- ① From (4), • If  $R_f = R_1$ ,  $V_o = -V_i$  or  $\frac{V_o}{V_i} = -1 = A_v$   
amplifier is unity gain inverting amplifier.
- ② From (7), • Irrespective of the value of  $R_1$  &  $R_f$ ,  $V_o \geq V_i$   
• If  $R_f = 0$  or  $R_1 = \infty$ , then  $V_o = V_i$ , amplifier is unity gain non-inverting amplifier.
- ③ From (8), • If  $R_1 = R_2 = R_3 = R_f$ , then,  $V_o = -(V_1 + V_2 + V_3)$   
output voltage is the negative of the sum of the input voltages [Gain of the Summer is unity (1)]  
• If  $R_1 = R_2 = R_3 = 3R_f$ , then,  $V_o = - \left( \frac{V_1 + V_2 + V_3}{3} \right)$   
or  $R_1 = R_2 = 2R_f$  &  $V_3 = 0$ , then  $V_o = - \left( \frac{V_1 + V_2}{2} \right)$   
then circuit is averager or averaging circuit

### ⑤ Non-inverting Summer:

Definition: An op-amp circuit, in which the output voltage is the sum of the input voltages is called Non-inverting Summer.

Circuit diagram:

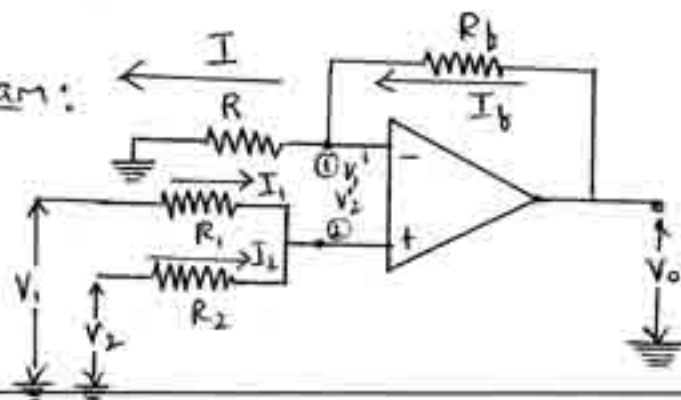



Analysis:

APPLYING KCL at node ②

$$I_1 + I_2 = 0 \quad (\text{No current flows into input})$$






$$\Rightarrow \frac{V_1 - V_2'}{R_1} + \frac{V_2 - V_2'}{R_2} = 0$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} = V_2' \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow \frac{R_2 V_1 + R_1 V_2}{R_1 R_2} = V_2' \left( \frac{R_2 + R_1}{R_1 R_2} \right)$$

$$\Rightarrow V_2' = \frac{R_2 V_1 + R_1 V_2}{R_1 + R_2} \quad \text{--- (9)}$$

Wave forms

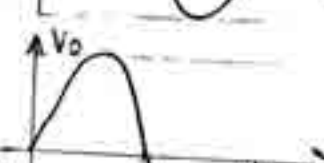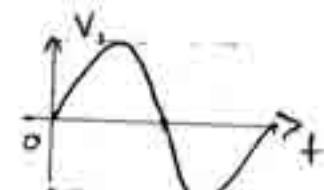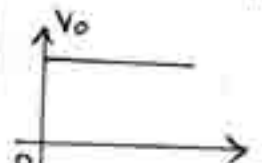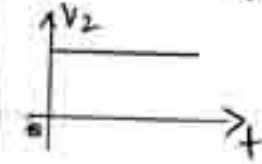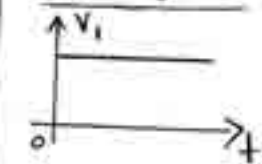

APPLYING KCL at node ①.

$$I_b = I$$

$$\Rightarrow \frac{V_0 - V_1'}{R_b} = \frac{V_1' - 0}{R}$$

$$\Rightarrow \frac{V_0}{R_b} = V_1' \left( \frac{1}{R} + \frac{1}{R_b} \right)$$

$$\Rightarrow \frac{V_0}{R_b} = V_1' \left( \frac{R_b + R}{R R_b} \right)$$

$$V_0 = V_1' \left( \frac{R + R_b}{R} \right) \quad \text{--- (10)}$$

$$\left( \text{From Virtual Ground, } V_1' = V_2' = \frac{R_2 V_1 + R_1 V_2}{R_1 + R_2} \right)$$

$$\Rightarrow V_0 = \left( \frac{R_2 V_1 + R_1 V_2}{R_1 + R_2} \right) \left( \frac{R + R_b}{R} \right)$$

$$\Rightarrow V_0 = \frac{R_2 (R + R_b)}{R (R_1 + R_2)} V_1 + \frac{R_1 (R + R_b)}{R (R_1 + R_2)} V_2$$

$$\Rightarrow \boxed{V_0 = \frac{(1 + R_b/R)}{(1 + R_1/R_2)} V_1 + \frac{(1 + R_b/R)}{(1 + R_2/R_1)} V_2} \quad \text{--- (11)}$$

### Conclusion:

From (11), the output voltage is proportional to the sum of the input voltages.


Note: (1) From (11). If  $R = R_f = R_1 = R_2$ ,  $V_o = V_1 + V_2$

Output voltage is equal to the non-inverted sum of the input voltages (2) From (8), if  $V_1, V_2, V_3$  are negative,  $V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3$

### \* (5) Subtractor @ Difference amplifier

Definition: An op-amp circuit, in which the output voltage is the difference (subtraction) of two input voltages is called Subtractor.

Circuit diagram:

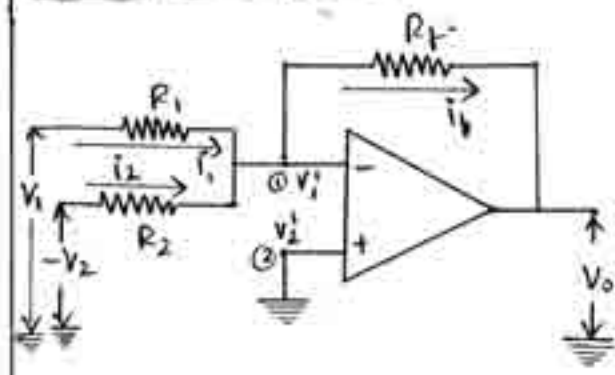

Applying KCL at node (1).

$$i_1 + i_2 = i_f$$


$$\Rightarrow \frac{V_1 - V_1'}{R_1} + \frac{-V_2 - V_1'}{R_2} = \frac{V_1' - V_o}{R_f}$$

$$\Rightarrow \frac{V_1}{R_1} - \frac{V_2}{R_2} = -\frac{V_o}{R_f} \quad (\because V_1' = V_2' = 0)$$

$$\Rightarrow \boxed{V_o = \frac{R_f}{R_2} V_2 - \frac{R_f}{R_1} V_1} \quad (12)$$


If  $R_1 = R_2 = R_f$ , then

$$\boxed{V_o = V_2 - V_1} \quad (13)$$

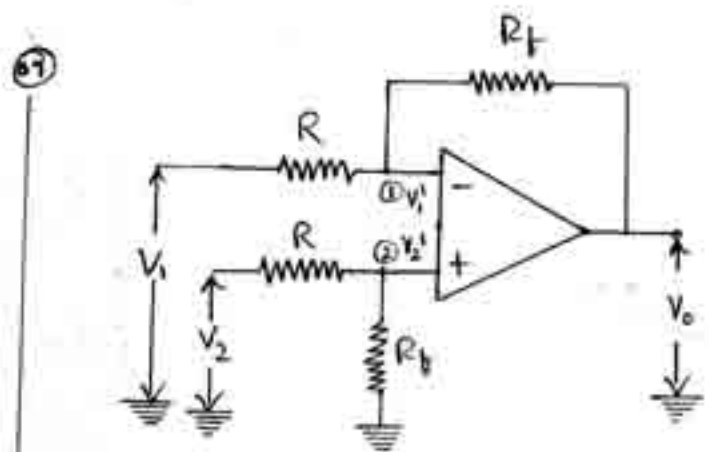

Let us use Superposition theorem.

Case (i): Let  $V_2 = 0$

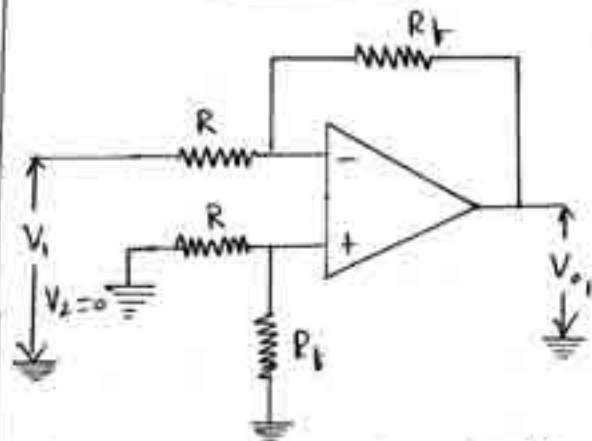

The resulting circuit is inverting amplifier

$$\therefore V_o = -\frac{R_f}{R} V_1 \quad (14)$$

Case (ii): Let  $V_1 = 0$

The resulting circuit is shown in fig (\*)

The circuit is non-inverting amplifier.

$$\therefore V_{o2} = \left(1 + \frac{R_f}{R}\right) V_2' \quad (15)$$

From Potential divider rule

$$V_2' = \frac{V_2 R_f}{R + R_f} \quad (16)$$

Using (16) in (15). We get

$$\begin{aligned} V_{o2} &= \left(1 + \frac{R_f}{R}\right) V_2 \left(\frac{R_f}{R + R_f}\right) \\ &= \left(\frac{R + R_f}{R}\right) V_2 \left(\frac{R_f}{R + R_f}\right) \end{aligned}$$

$$V_{o2} = \frac{R_f}{R} V_2 \quad (17)$$


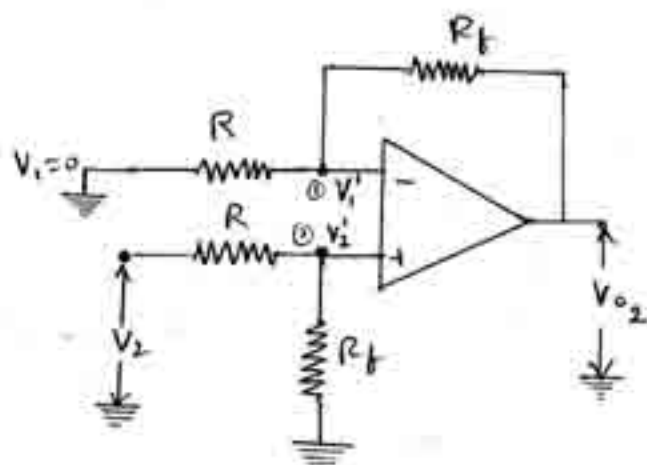


Fig (\*):

Voltage @ Potential divider rule

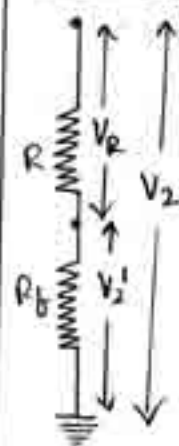

Voltage across  $R_f$

$$V_2' = \frac{V_2 \times R_f}{R + R_f}$$

Voltage across  $R$

$$V_R = \frac{V_2 R}{R + R_f}$$


From Superposition theorem, the output voltage is

$$\begin{aligned} V_o &= V_{o1} + V_{o2} \\ &= -\frac{R_f}{R} V_1 + \frac{R_f}{R} V_2 \end{aligned}$$

$$V_o = \frac{R_f}{R} (V_2 - V_1) \quad (18)$$

If  $R = R_f$ , then

$$V_o = V_2 - V_1 \quad (19)$$

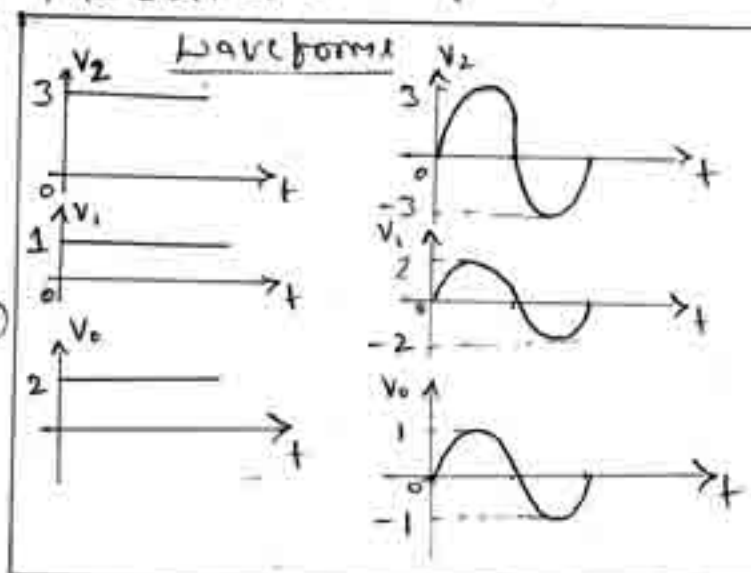


Conclusion: From (13) to (19), the output voltage is the difference of the two input voltages.

### \* ⑥ Differentiator:

Definition: An op-amp circuit, in which the output voltage is the differentiation (derivative) of the input voltage is called differentiator.

Circuit diagram

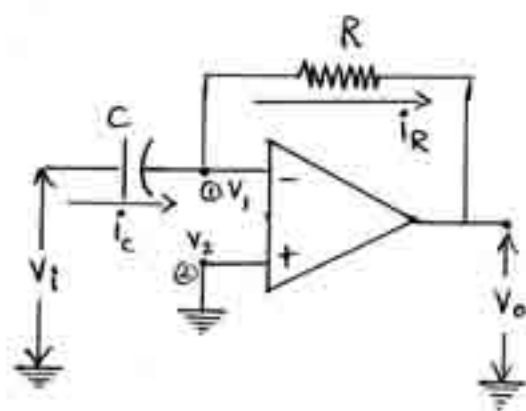

Analysis:

Applying KCL at node ①.

$$i_c = i_R$$

$$C \frac{d(V_i - V_1)}{dt} = \frac{V_1 - V_o}{R}$$

$$\Rightarrow C \frac{dV_i}{dt} = -\frac{V_o}{R} \quad \left( \because \text{From virtual ground concept } V_1 = V_2 = 0 \right)$$


$$\Rightarrow \boxed{V_o = -RC \frac{dV_i}{dt}} \quad \text{--- (20)}$$

Conclusion: From (20), the output voltage is proportional to the time derivative of the input voltage.

### \* ⑦ Integrator:

Definition: An op-amp circuit, in which the output voltage is the integration of the input voltage is called integrator.

Circuit diagram:

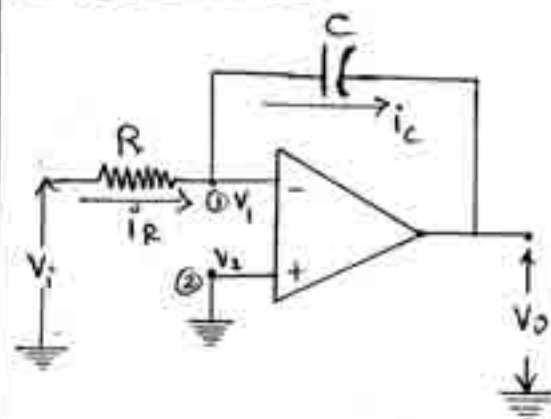

Analysis:

Applying KCL at node ①.

$$i_R = i_c$$

$$\frac{V_i - V_1}{R} = C \frac{d(V_1 - V_o)}{dt}$$

$$\Rightarrow \frac{V_i}{R} = -C \frac{dV_o}{dt} \quad \left( \text{From virtual ground concept, } V_1 = V_2 = 0 \right)$$

$$\Rightarrow dV_o = -\frac{1}{RC} V_i dt$$

Integrating on both sides.

$$V_o = -\frac{1}{Rc} \int_0^t V_i dt + V_o(0) \quad \text{--- (21)}$$












Where,  $V_o(0) \rightarrow$  Initial Voltage on capacitor at  $t=0$   
(Constant of integration)

If  $V_o(0)=0$ , then


$$V_o = -\frac{1}{Rc} \int_0^t V_i dt \quad \text{--- (22)}$$

Conclusion: From (21) & (22), the output voltage is Proportional to the integral of the input voltage.

Note: Waveforms

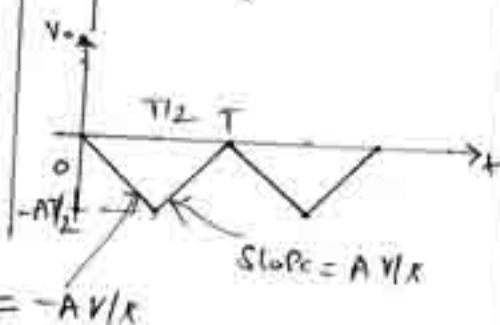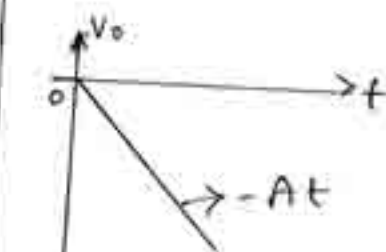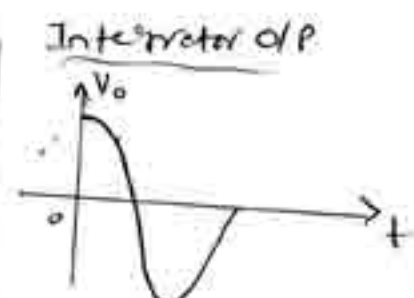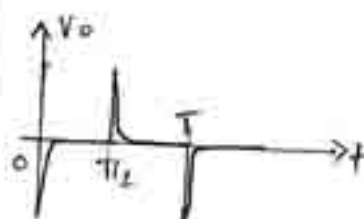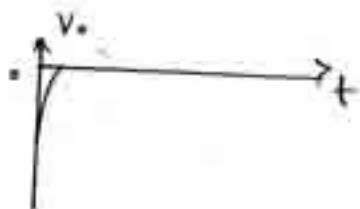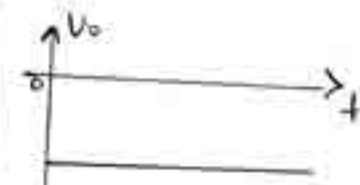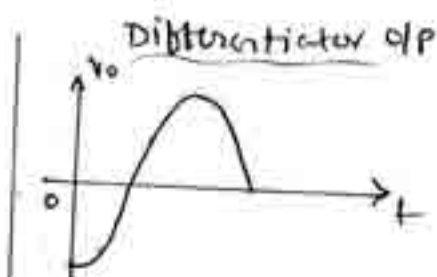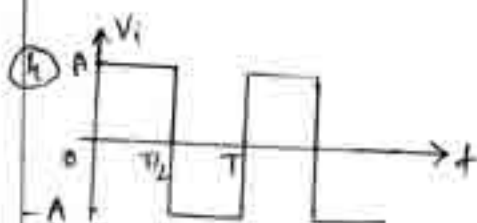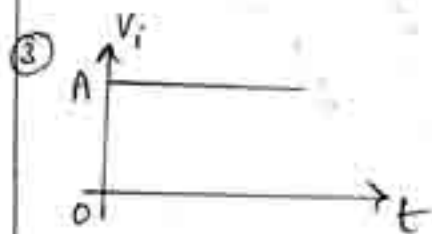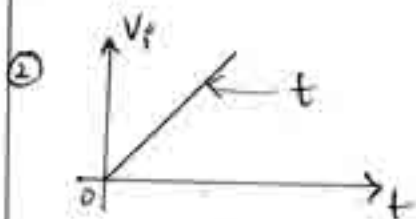
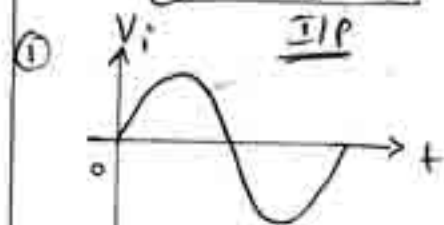




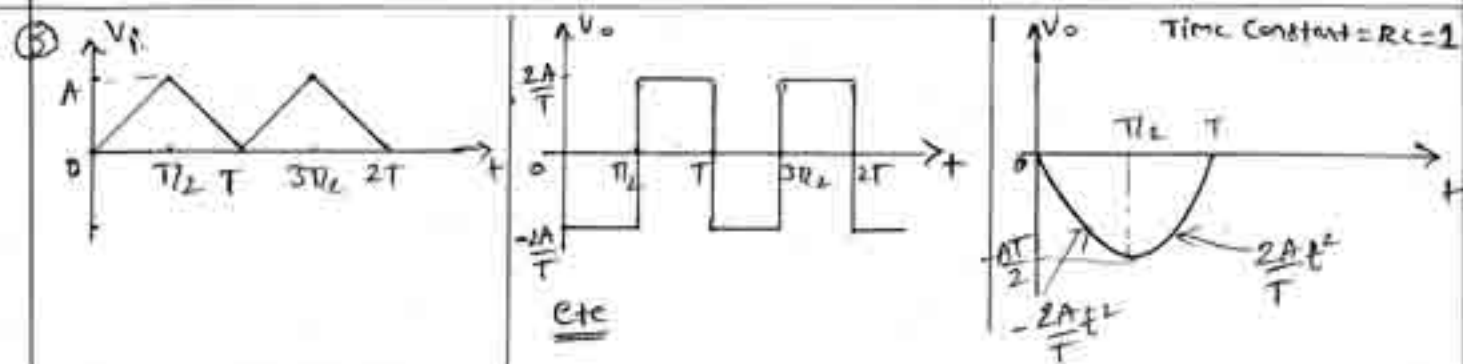

## II Ideal Voltage transfer characteristic of an op-amp

The output voltage,  
 $V_o = A V_d$

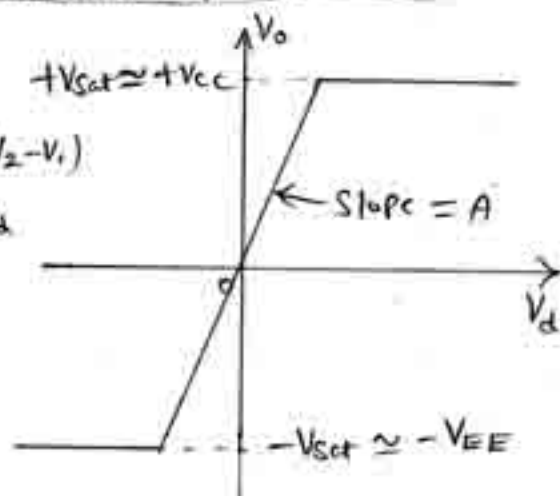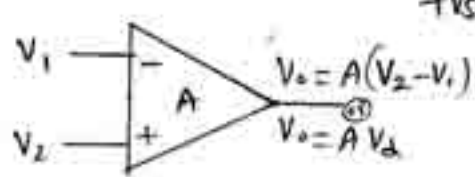


Fig(1):

Fig(1): Ideal Voltage transfer characteristic of an op-amp

## III Need for an op-amp

Let two signals  $V_1$  &  $V_2$  to be summed at node A in fig(2)

Applying KCL at node A

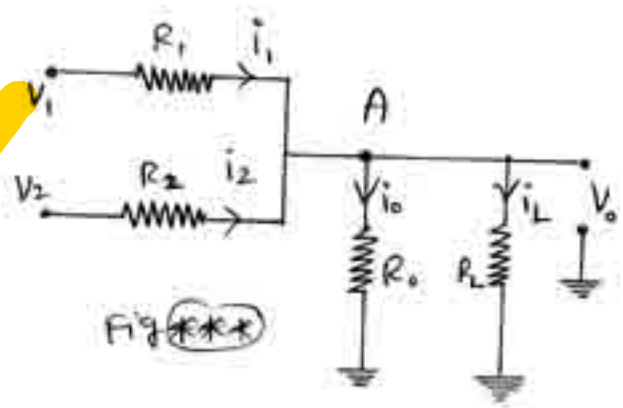

Fig(2)

$$i_1 + i_2 = i_o + i_L$$

$$\Rightarrow \frac{V_1 - V_o}{R_1} + \frac{V_2 - V_o}{R_2} = \frac{V_o}{R_o} + \frac{V_o}{R_L}$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} = V_o \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_o} + \frac{1}{R_L} \right]$$

$$\Rightarrow V_o \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_P} \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$\Rightarrow V_o \left[ 1 + \frac{R_p}{R_1} + \frac{R_p}{R_2} \right] = V_1 \left( \frac{R_p}{R_1} \right) + V_2 \left( \frac{R_p}{R_1} \right) \quad \left[ \text{Where } R_p = \frac{1}{\frac{1}{R_o} + \frac{1}{R_L}} \right]$$

$\Rightarrow$

$$V_o = \frac{V_1 \left( \frac{R_p}{R_1} \right) + V_2 \left( \frac{R_p}{R_1} \right)}{\left[ 1 + \frac{R_p}{R_1} + \frac{R_p}{R_2} \right]}$$

— (\*)

From eqn (\*), it is clear that  $V_o$  depends on  $R_p$  which in turn depends on  $R_L$ .

It is desirable to make  $V_o$  independent of  $R_L$ . This is possible if  $R_o \ll R_L$  @  $\frac{1}{R_o} \gg \frac{1}{R_L}$  ( $R_p \approx \frac{1}{R_o}$ )

But  $R_p$  will be small, results in small value of  $V_o$  which is undesirable. Therefore it is necessary to use amplifier whose gain (@ output voltage) is independent of  $R_L$ .

Thus op-amp is preferred since closed loop voltage gain (@ output voltage) is independent of  $R_L$  (depends only on external resistors  $R_f$  &  $R_i$ ).

- ① For an inverting amplifier  $R = 10\text{ k}\Omega$  &  $R_f = 60\text{ k}\Omega$ . What is the output voltage for  $V_i = 2\text{ V}$ ?

Sol: Given  $R = 10\text{ k}\Omega$ ,  $R_f = 60\text{ k}\Omega$ ,  $V_i = 2\text{ V}$ ,  $V_o = ?$

For an inverting amplifier,

$$V_o = -\frac{R_f}{R} V_i = -\frac{60 \times 10^3}{10 \times 10^3} (2) = \underline{\underline{-12\text{ V}}}$$

- ② Design an inverting amplifier for output voltage of  $-10\text{ V}$  & an input voltage of  $1\text{ V}$ .

Sol: Given  $V_o = -10\text{ V}$ ,  $V_i = 1\text{ V}$ ,  $R_i = ?$ ,  $R_f = ?$

For an inverting amplifier,


$$V_o = -\frac{R_f}{R_i} V_i$$

$$\Rightarrow -10 = -\frac{R_f (1)}{R_i}$$

$$\Rightarrow \frac{R_f}{R_i} = 10$$

Assume  $R_i = 1\text{ k}\Omega //$

$\therefore R_f = 10\text{ k}\Omega //$

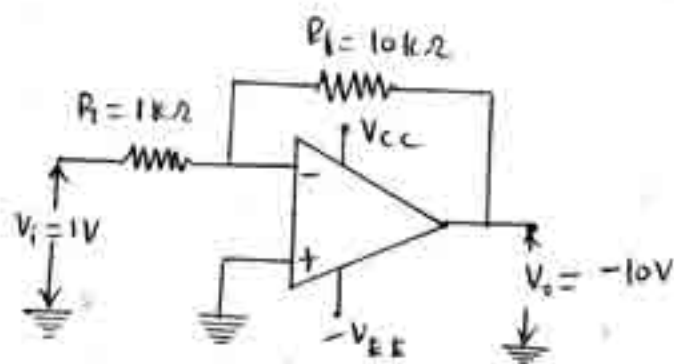

- ③ The output signal of an op-amp with a slew-rate of  $5\text{ V}/\mu\text{s}$  has a maximum value of  $15\text{ V}$ . Find the max freq for undistorted output voltage.

Sol: Given  $SR = 5\text{ V}/\mu\text{s}$ ,  $V_m = 15\text{ V}$ ,  $f_{\text{max}} (\omega_{\text{max}}) = ?$

We have  $f_{\text{max}} = \frac{SR}{2\pi V_m}$   $\therefore \omega_{\text{max}} = \frac{SR}{V_m}$

$$= \frac{5/10^{-6}}{2\pi (15)} \quad \omega_{\text{max}} = \frac{5/10^{-6}}{15}$$

$$f_{max} = 53.05 \text{ KHz} \quad \text{②} \quad L_{max} = 333.33 \text{ rad/s}$$

- ④ Determine the output voltage of an op-amp for the input voltages of  $0.05 \text{ mV}$  &  $0.04 \text{ mV}$ . The differential gain of the amplifier is  $50000$  &  $\text{CMRR} = 2 \times 10^5$ .

Sol: Given  $V_o = ?$ ,  $V_1 = 0.05 \text{ mV}$ ,  $V_2 = 0.04 \text{ mV}$ ,  $A_d = 50000$ ,  
 $\text{CMRR} = 2 \times 10^5$

We have,

$$V_o = A_d V_d + A_c V_c$$


$$= 50000 \times 10 \times 10^{-6} + 0.25 \times 45 \times 10^{-6}$$

$$= 0.5 + 11.25 \times 10^{-6}$$

$$= 500.011 \text{ mV}$$

$$\begin{aligned} \therefore V_d &= V_1 - V_2 \\ &= 0.05 \times 10^{-3} - 0.04 \times 10^{-3} \\ &= 0.01 \times 10^{-3} = 10 \times 10^{-6} \\ A_c &= \frac{A_d}{\text{CMRR}} = \frac{50000}{2 \times 10^5} = 0.25 \end{aligned}$$

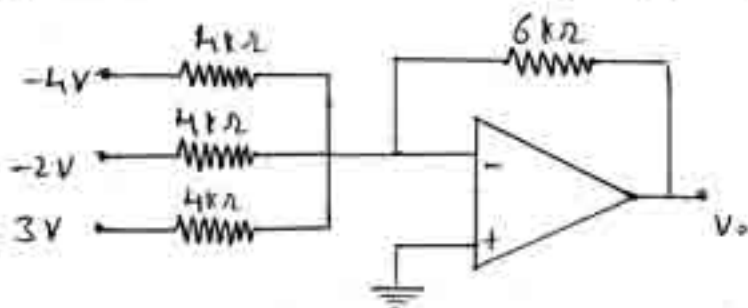- ⑤ Find the output voltage for the circuit shown in fig ⑤



Sol: We have,

$$\begin{aligned} V_o &= -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right) \\ &= -\frac{R_f}{R_i} (V_1 + V_2 + V_3) \quad (\because R_1 = R_2 = R_3 = 4 \text{ k}\Omega) \\ &= -\frac{6 \text{ k}\Omega}{4 \text{ k}\Omega} (-4 - 2 + 3) \\ &= 4.5 \text{ V} \end{aligned}$$

6) Design an adder circuit for  $V_o = -(2V_1 + 3V_2 + 5V_3)$

Sol: Given  $V_o = -(2V_1 + 3V_2 + 5V_3)$


Comparing With,  $V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$

$$\frac{R_f}{R_1} = 2, \quad \frac{R_f}{R_2} = 3, \quad \frac{R_f}{R_3} = 5$$

Let  $R_f = 100k\Omega$

$$\therefore R_1 = \frac{R_f}{2}, \quad R_2 = \frac{R_f}{3}, \quad R_3 = \frac{R_f}{5}$$
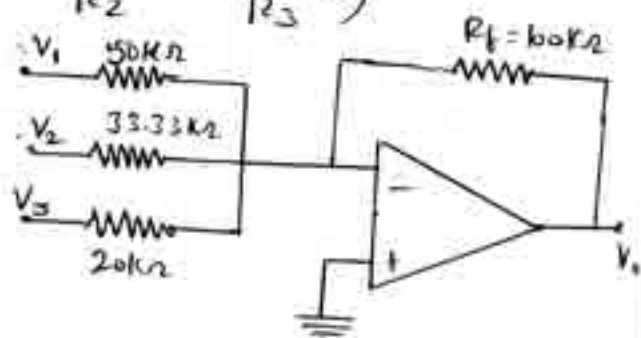
$$\Rightarrow \underline{R_1 = 50k\Omega} \quad \underline{R_2 = 33.33k\Omega} \quad \underline{R_3 = 20k\Omega}$$



7) Design an adder circuit for  $V_o = 3V_1 + 2V_2 - 4V_3$

Sol: Given  $V_o = 3V_1 + 2V_2 - 4V_3$

$$\Rightarrow V_o = -[3(-V_1) + 2(-V_2) + 4V_3]$$

Comparing With,


$$V_o = -\left[\frac{R_f}{R_1}(-V_1) + \frac{R_f}{R_2}(-V_2) + \frac{R_f}{R_3}V_3\right]$$

$$\frac{R_f}{R_1} = 3, \quad \frac{R_f}{R_2} = 2, \quad \frac{R_f}{R_3} = 4$$

Let  $R_f = 10k\Omega$

$$\therefore R_1 = \frac{10k}{3}, \quad R_2 = \frac{10k}{2}, \quad R_3 = \frac{10k}{4}$$
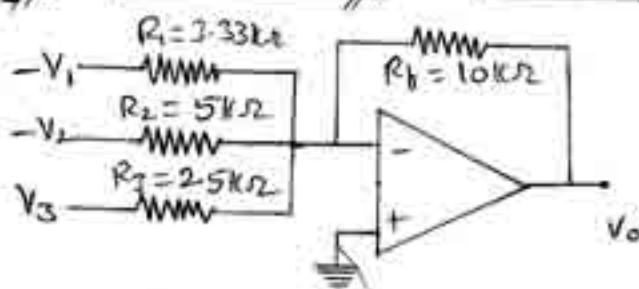
$$\boxed{R_1 = 3.33k\Omega} \quad \boxed{R_2 = 5k\Omega} \quad \boxed{R_3 = 2.5k\Omega}$$









8) A differential amplifier has open circuit gain of  $10^4$ , the input signals are  $1.2 \text{ mV}$  &  $2.4 \text{ mV}$ . Determine the output voltage.


Sol: Given  $A_d = 10^4$ ,  $V_2 = 2.4 \times 10^{-6} \text{ V}$ ,  $V_1 = 1.2 \times 10^{-6} \text{ V}$ ,  $V_o = ?$

Output Voltage,  $V_o = A_d V_d$   
 $= A_d (V_2 - V_1)$  ( $\because$  since  $A_c$  is not given)  
 $= 10^4 (2.4 - 1.2) \times 10^{-6}$   
 $= \underline{\underline{0.012 \text{ V}}}$

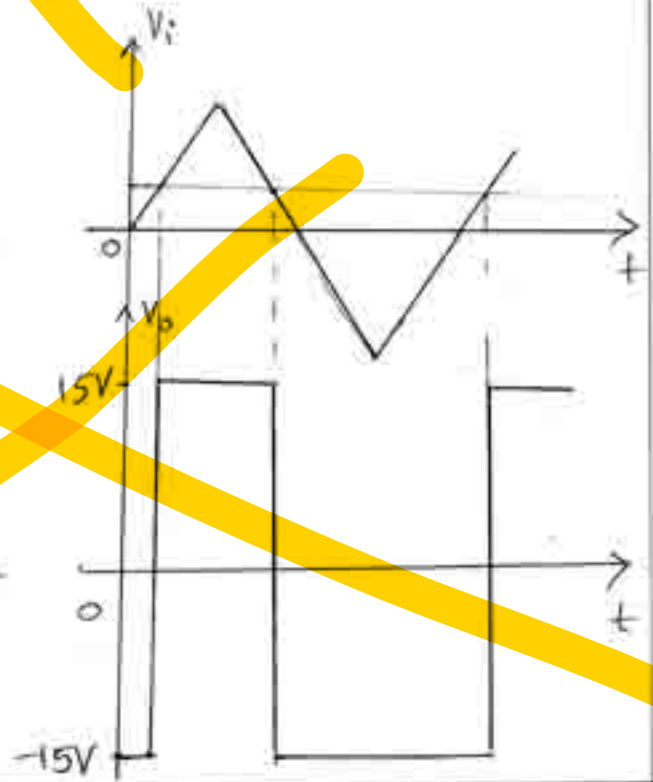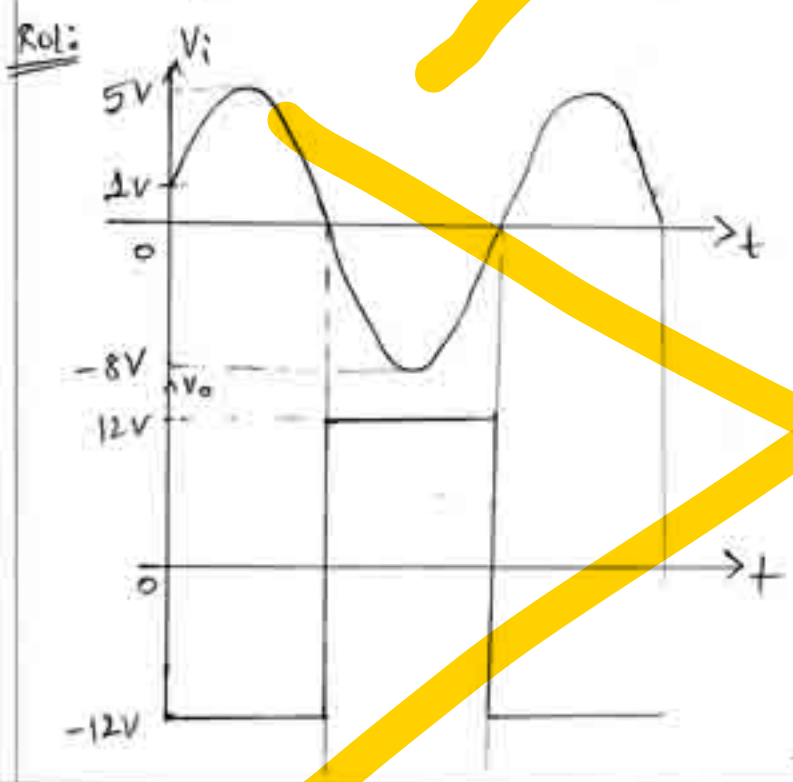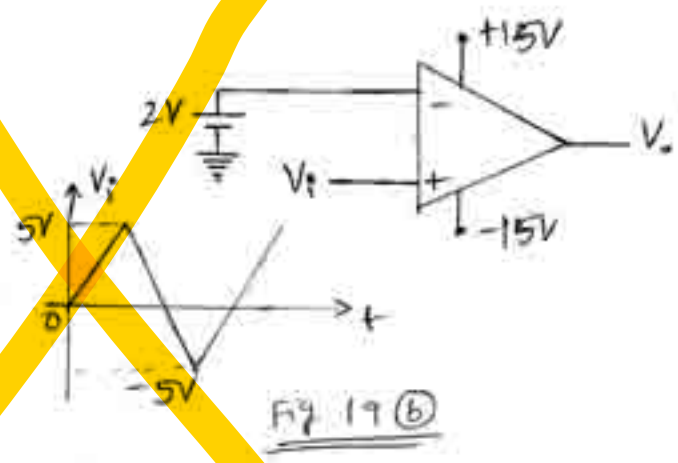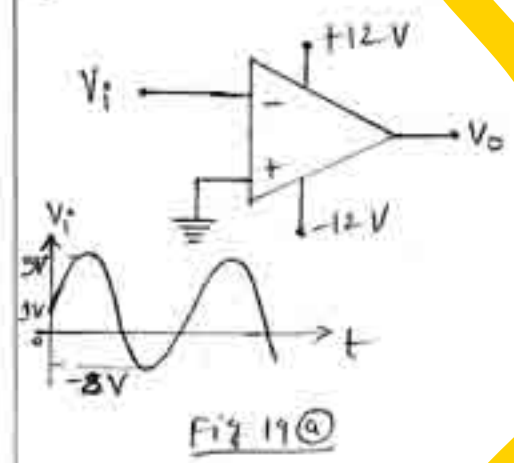
9) For the circuit shown in fig 19(a), draw the output voltage for the input voltage shown in fig 19(b)



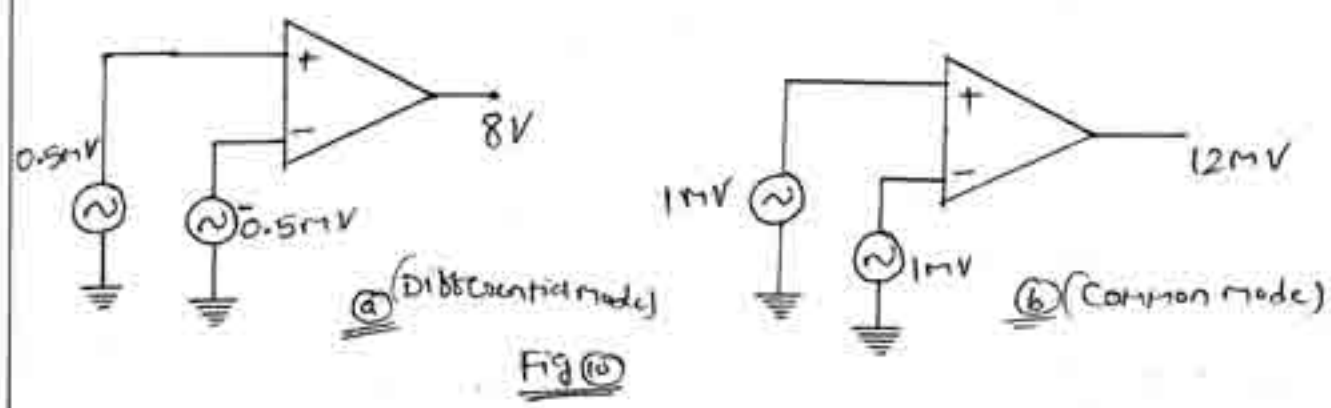10) Calculate the CMRR for the circuit measurements shown in fig 10.



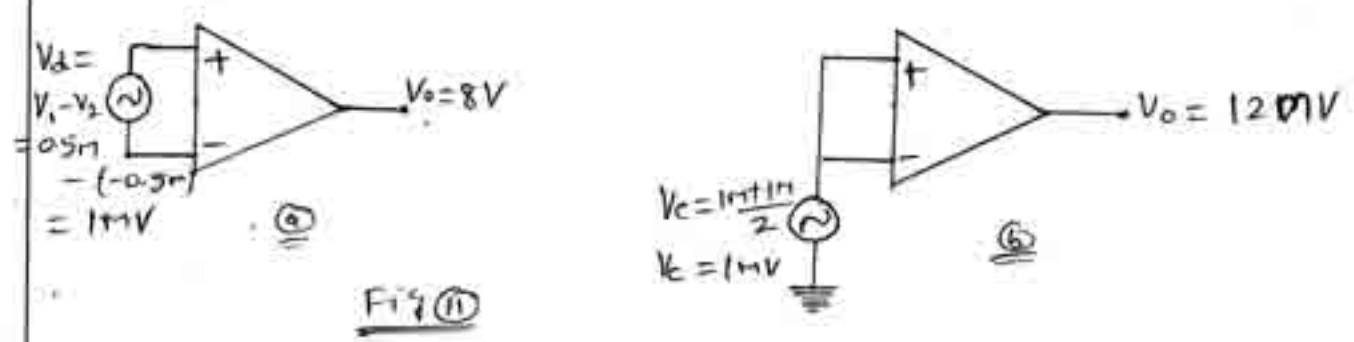Rel:  
Fig 10(a) can be redrawn as shown in fig 11(a) & fig 10(b) can be redrawn as shown in fig 11(b).



From fig 11(a),

$$A_d = \frac{V_o}{V_d} = \frac{8}{1 \times 10^{-3}} = 8000$$

From fig 11(b),

$$A_c = \frac{V_o}{V_c} = \frac{12 \times 10^{-3}}{1 \times 10^{-3}} = 12$$

$\therefore$  CMRR is,  $CMRR = \frac{A_d}{A_c} = \frac{8000}{12} = 666.66$

$CMRR (dB) = 20 \log_{10} \frac{A_d}{A_c} = 20 \log_{10} (666.66) = 56.47 dB$

11) Determine the output voltage of an OP-amp for input voltages of  $V_{i1} = 150mV$ ,  $V_{i2} = 140mV$ . The amplifier has a differential gain of  $A_d = 4000$  & the value of CMRR is:  
 (a) 100 (b)  $10^5$

Rel: Difference voltage,  $V_d = V_{i1} - V_{i2} = 150 \times 10^{-6} - 140 \times 10^{-6} = 10mV$   
 Common mode voltage,  $V_c = \frac{V_{i1} + V_{i2}}{2} = \frac{150 \times 10^{-6} + 140 \times 10^{-6}}{2} = 145mV$

④ We have,  $V_o = A_d V_d \left( 1 + \frac{1}{CMRR} \frac{V_c}{V_d} \right)$

$$= (4000) (10 \times 10^{-6}) \left( 1 + \frac{1}{100} \frac{145 \times 10^{-6}}{10 \times 10^{-6}} \right)$$

$$= 40 \times 10^{-3} (1 + 0.145)$$

$$= \underline{45.8 \text{ mV}}$$

⑤  $V_o = (4000) (10 \times 10^{-6}) \left( 1 + \frac{1}{10^5} \frac{145 \times 10^{-6}}{10 \times 10^{-6}} \right)$

$$= 40 \times 10^{-3} (1.000145)$$

$$= \underline{40.0058 \text{ mV}}$$

⑫ Calculate the output voltage of a non-inverting amplifier for  $V_i = 2 \text{ V}$ ,  $R_f = 500 \text{ k}\Omega$  &  $R_i = 100 \text{ k}\Omega$

Sol: Given  $V_i = 2 \text{ V}$ ,  $R_f = 500 \text{ k}\Omega$ ,  $R_i = 100 \text{ k}\Omega$ ,  $V_o = ?$

For non-inverting amplifier,

$$V_o = \left( 1 + \frac{R_f}{R_i} \right) V_i = \left( 1 + \frac{500 \times 10^3}{100 \times 10^3} \right) 2 = 8(2) = \underline{12 \text{ V}}$$

⑬ A 741C is an OP-amp with  $A = 100,000$  & a minimum  $CMRR_{dB} = 70 \text{ dB}$ . What is the common-mode voltage gain? If a desired & common-mode signal each has a value of  $5 \text{ mV}$ , what is the output voltage?

Sol: Given  $A = A_d = 100,000$ ,  $CMRR_{dB} = 70 \text{ dB}$ ,  $A_c = ?$

$V_c = 5 \times 10^{-6} \text{ V}$ ,  $V_o = ?$

We have  $CMRR_{dB} = 20 \log_{10} \frac{A}{A_c}$

$$\Rightarrow 70 = 20 \log_{10} \frac{A}{A_c}$$

$$\Rightarrow \frac{A}{A_c} = 10^{70/20}$$

$$\Rightarrow A_c = \frac{A}{10^{7/2}} = \frac{100,000}{10^{3.5}} = \underline{31.622}$$


We have

$$V_o(\text{CM}) = A_c V_c$$

$$= 31.622 \times 5 \times 10^{-6}$$

$$V_o(\text{CM}) = \underline{\underline{158.11 \text{ mV}}}$$

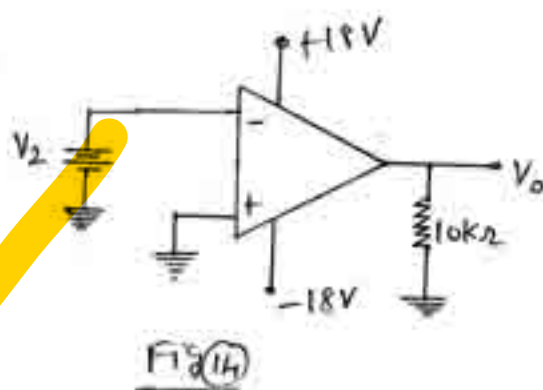- ④ Assume that negative saturation occurs at  $1V$  less than the supply voltage with an op-amp. How much inverting input voltage does it take to drive the op-amp of fig (14) into negative saturation?



Sol: Given  $V_{cc} = \pm 18V$ , Negative Saturation Voltage =  $-17V$   
 $V_2 = ?$   $A = 2 \times 10^5$  (Assume)

Given negative Saturation Voltage =  $-17V$ , Output saturates negatively at  $-17V$ .

$$\therefore V_2 = \frac{17}{200,000} = \underline{\underline{85 \mu V}} \quad \left[ \because V_o = A V_2 \right]$$

- ⑤ The input voltage to an op-amp is a large voltage step. The output is an exponential waveform that changes  $0.75V$  in  $50ns$ . What is the Slew rate of the op-amp?

Sol: Given  $dV = 0.75V$ ,  $dt = 50ns$

$$\text{We have, } SR = \frac{dV}{dt} = \frac{0.75}{50 \times 10^{-9}} = \underline{\underline{15V/\mu s}}$$

- ⑥ An op-amp has Slew rate of  $8V/\mu s$ . What is the Power bandwidth for a Peak output voltage of  $5V$ ?


Sol: Given  $SR = 8V/\mu s$ ,  $V_m = 5V$ ,  $f_{max} = ?$

Highest  $f_{max}$  @ Power bandwidth,



$$f_{max} = \frac{SR}{2\pi V_M} = \frac{.8/10^6}{2\pi \times 5} = \underline{\underline{254.64 \text{ KHz}}}$$

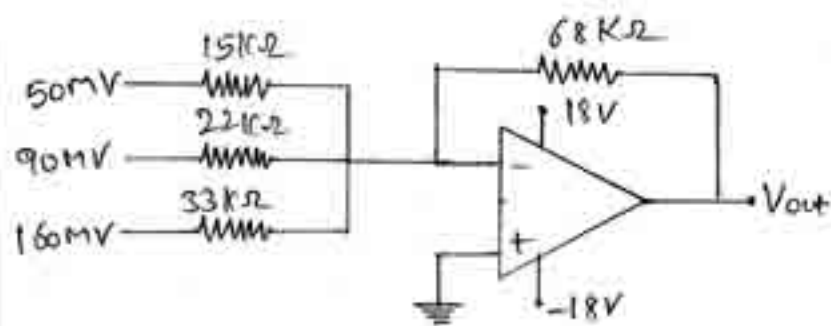17 In fig 17. What is the ac output Voltage? If a Compensating resistor needs to be added to non-inverting input, what size should it be?



sol:

AC output Voltage,

$$\begin{aligned} V_o &= \left( \frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} + \frac{R_f V_3}{R_3} \right) \\ &= \left[ \frac{68K (50 \times 10^{-3})}{15K} + \frac{68K (90 \times 10^{-3})}{22K} + \frac{68K (160 \times 10^{-3})}{33K} \right] \\ &= \underline{\underline{834.53 \text{ mV}}} \end{aligned}$$

Compensating resistor,

$$\begin{aligned} R_c &= R_1 \parallel R_2 \parallel R_3 \\ &= \frac{1}{\frac{1}{15K} + \frac{1}{22K} + \frac{1}{33K}} \\ &= \underline{\underline{7.02 \text{ K}\Omega}} \end{aligned}$$

If a Summing circuit needs to be compensated by adding an equal resistance to the non-inverting input, the resistance is the Thevenin resistance looking from the inverting input back to the sources

18 What is the initial Slope of a Sine Wave With a frequency of 15KHz & a Peak Value of 2V? What happens to the initial Slope if the frequency increases to 30KHz?

Q1: Given (a)  $f = 15 \text{ kHz}$ ,  $V_m = 2 \text{ V}$ ,  $S_s(SR) = ?$

Initial slope of a sine wave.

$$S_s = 2\pi f V_m$$

$$= 2\pi \times 15 \times 10^3 \times 2$$

$$= 188.49 \text{ mV/}\mu\text{s}$$

$$(\because SR = S_s = 2\pi f V_m)$$

(b)  $f = 30 \text{ kHz}$ ,  $V_m = 2 \text{ V}$ ,  $S_s = ?$

$$S_s = 2\pi f V_m = 2\pi \times 30 \times 10^3 \times 2 = 376.99 \text{ mV/}\mu\text{s}$$

Q2: Find  $V_{out}$   
in fig (19), if  
 $R = 10 \text{ k}\Omega$ ,  $V_1 = -20 \text{ mV}$   
 $V_2 = -30 \text{ mV}$


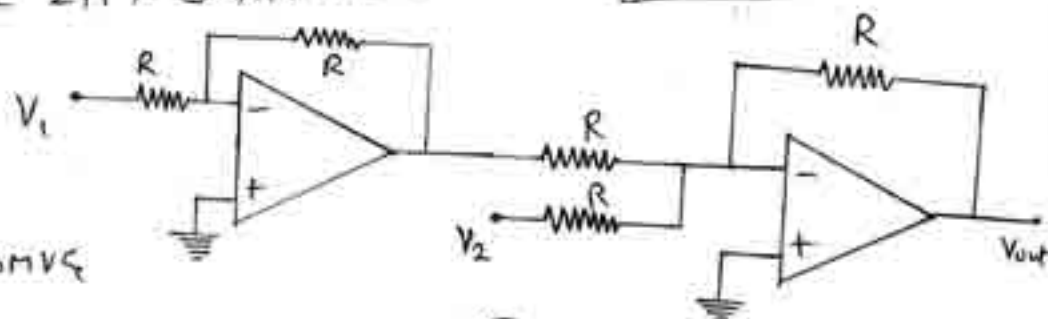
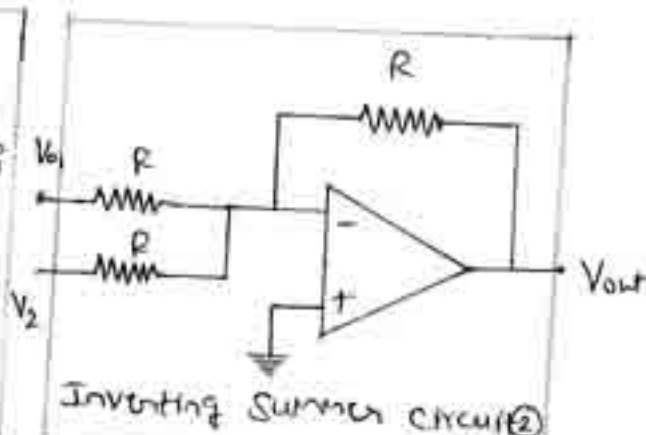


Fig (19)

Sol:

The given circuit is redrawn

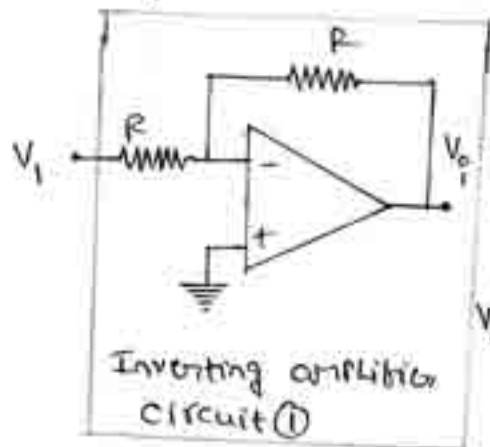

From circuit (1),

$$V_{01} = -\frac{R}{R} V_1$$

$$= -(-20 \text{ mV})$$

$$= 20 \text{ mV}$$

From circuit (2)

$$V_{out} = -\left(\frac{R}{R} V_{01} + \frac{R}{R} V_2\right)$$

$$= -(20 \text{ mV} - 30 \text{ mV})$$

$$= -20 \text{ mV} + 30 \text{ mV}$$


$$V_{out} = V_2 - V_{01}$$

$$V_{out} = 10 \text{ mV}$$

The given circuit is a subtractor



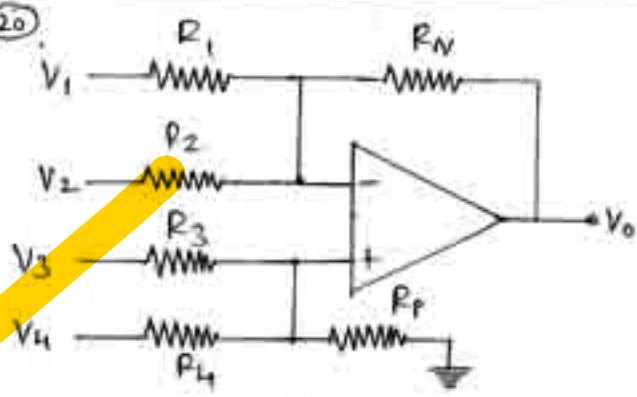2) In the op-amp circuit of fig(20).  
Show that  $V_o = (V_3 + V_4) - (V_1 + V_2)$   
if all resistances are equal.




Fig(20)

Sol:

Let us use Superposition theorem.

Case (i): Let  $V_2 = V_3 = V_4 = 0$

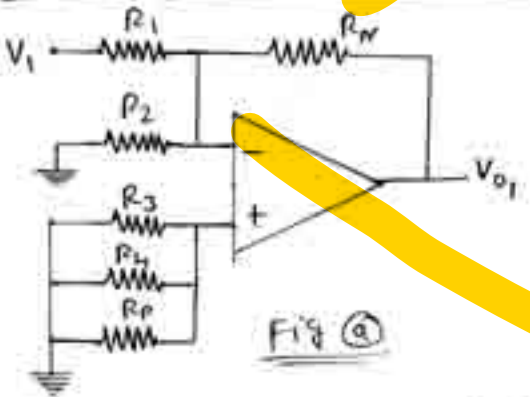


Fig(a)

The resulting circuit is shown in fig(a). The circuit is an inverting amplifier.  $\therefore V_o1 = -\frac{R_N}{R_1} V_1$

$$\boxed{V_{o1} = -V_1} \quad \text{(Let } R_1 = R_N) \quad \text{--- (1)}$$

Case (ii): Let  $V_1 = V_3 = V_4 = 0$

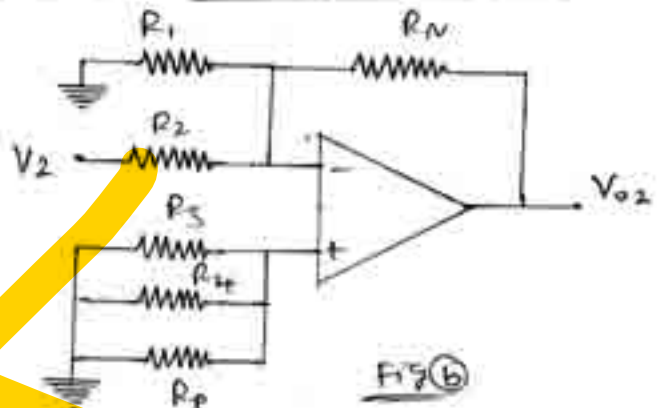


Fig(b)

The output voltage  $V_{o2}$  is,

$$V_{o2} = -\frac{R_N}{R_2} V_2$$

$$\boxed{V_{o2} = -V_2} \quad \text{--- (2) (Let } R_2 = R_N)$$

Case (iii): Let  $V_1 = V_2 = V_4 = 0$

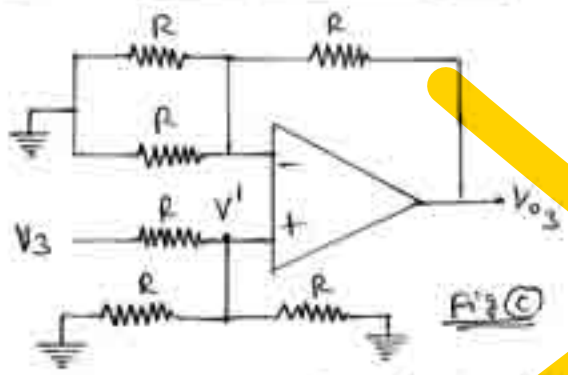


Fig(c)

From potential divider rule,

$$V' = \frac{V_3 (R \parallel R)}{R + (R \parallel R)}$$

Case (iv): Let  $V_1 = V_2 = V_3 = 0$

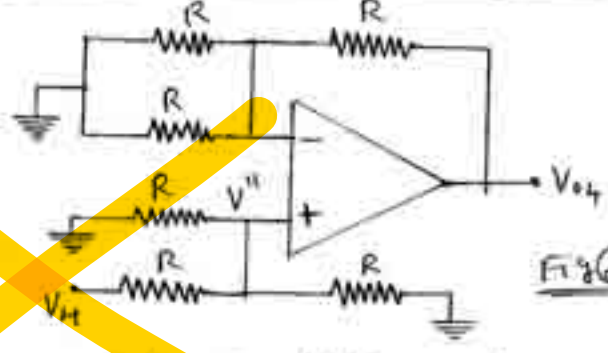

Fig(d)

From potential divider rule,

$$V'' = \frac{V_4 (R \parallel R)}{R + (R \parallel R)}$$


$$V' = V_3 \frac{\frac{RR}{R+R}}{R + \frac{RR}{R+R}}$$

$$= V_3 \frac{\frac{R^2}{2R}}{R + \frac{R^2}{2R}}$$

$$= V_3 \frac{R/2}{3R/2}$$

$$= \frac{V_3}{3} \quad \text{--- (4)}$$

Now Fig (c) can be redrawn as

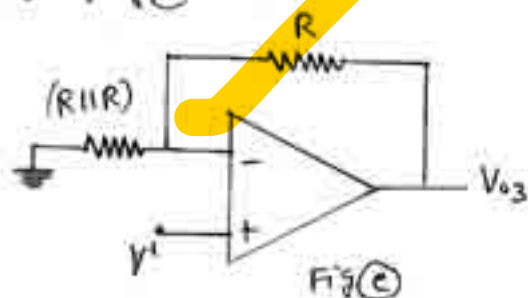

The resulting circuit shown in fig (c) is non-inverting amplifier.

∴ The output voltage  $V_{o3}$  is

$$V_{o3} = \left[ 1 + \frac{R}{(R||R)} \right] V' \quad \text{--- (5)}$$

Using (4) in (5),

$$V_{o3} = \left[ 1 + \frac{R}{(RR/R+R)} \right] \frac{V_3}{3}$$

$$= \left( 1 + \frac{R}{R^2/2R} \right) \left( \frac{V_3}{3} \right)$$

$$= (1+2) \frac{V_3}{3}$$

$$\boxed{V_{o3} = V_3} \quad \text{--- (6)}$$

$$\Rightarrow V'' = \frac{V_4 (RR/R+R)}{R + (RR/R+R)}$$

$$\Rightarrow V'' = \frac{V_4}{3} \quad \text{--- (7)}$$

$$V_{o4} = \left[ 1 + \frac{R}{(R||R)} \right] V''$$

$$\boxed{V_{o4} = V_4} \quad \text{--- (8)}$$

From Superposition theorem, the output voltage is

$$V_o = V_{o1} + V_{o2} + V_{o3} + V_{o4} = (V_3 + V_4) - (V_1 + V_2)$$

1) For the fig (2), determine  $V_o$ .


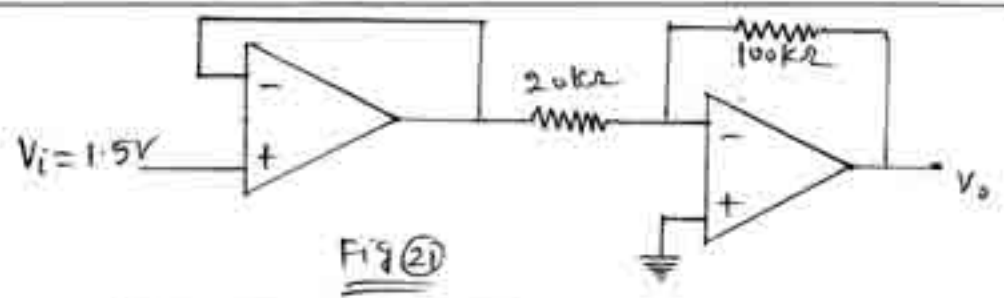


Fig (2)

Sol:

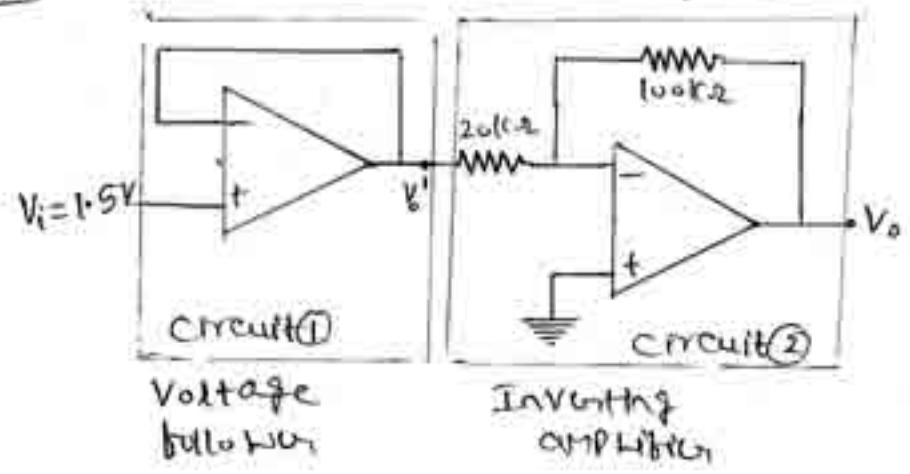

From circuit (1), o/p of voltage follower is,

$$V_o' = V_i = 1.5V$$

From circuit (2), output  $V_o$  is,

$$V_o = -\left(\frac{100K}{20K}\right) V_o' = -5(1.5) = -7.5V$$

2) Determine the input bias current and input offset current to an op-amp if the current into non-inverting and inverting terminals are 8.3mA and 7.9mA respectively.

Sol: Given  $I_1 = 8.3mA$ ,  $I_2 = 7.9mA$ ,  $I_{ib} = ?$ ,  $I_{io} = ?$

Input bias current,  $I_{ib} = \frac{I_1 + I_2}{2} = \frac{8.3 + 7.9}{2} = 8.1mA$

Input offset current,  $I_{io} = |I_1 - I_2| = |8.3 - 7.9| = 0.4mA$

3) How long does it take the output voltage of an op-amp to go from -8V to 7V, if the Slew rate is 0.5V/μs?

Sol: Given  $dV_o = 7 - (-8) = 15V$ ,  $SR = \frac{0.5}{10^{-6}} V/\mu s$ ,  $dt = ?$

We have  $SR = \frac{dV_o}{dt} \Rightarrow dt = \frac{dV_o}{SR} = \frac{15}{0.5/10^{-6}} = 30\mu s$

4) For the inverting amplifier,  $R_i = 20k\Omega$ ,  $R_f = 100k\Omega$ ,  $V_{in} = 1mV$ , calculate

- Ⓐ closed-loop gain Ⓑ Input resistance seen by source  
 Ⓒ output voltage Ⓓ Input current Ⓔ current entering the op-amp input terminals Ⓕ current through feedback

Sol: Given,  $R_i = 20k\Omega$ ,  $R_f = 100k\Omega$ ,  $V_{in} = 1mV$ ,  $A$  (or  $A_d$ ) = ?

$$R_{in} = ? , I_{in} = ? , V_o = ? , I_{op-amp} = ? , I_f = ?$$

Ⓐ We have,

$$A = -\frac{R_f}{R_i} = -\frac{100 \times 10^3}{20 \times 10^3} = -5$$

Ⓑ  $R_{in} = R_i = 20k\Omega$

Ⓒ Output Voltage,  $V_o = +A V_{in} = -5 \times 1 \times 10^{-3} = -5mV$

Ⓓ  $I_{in} = \frac{V_{in} - V_i}{R_i} = \frac{1 \times 10^{-3} - 0}{20 \times 10^3} = 50nA$  [∵ From virtual ground,  $V_i = V_2 = 0$ ]

Ⓔ  $I_{op-amp} = 0$  (∵ No current flows into op-amp input terminals)

Ⓕ  $I_f = I_{in} = 50nA$

5) A sinusoidal signal with peak value  $6mV$  & of  $20kHz$  is applied to the input of an ideal op-amp integrator with  $R = 100k\Omega$  &  $C = 1nF$ . Find the output voltage.

Sol: Given  $R = 100k\Omega$ ,  $C = 1nF$ ,  $V_m = 6mV$ ,  $f = 20kHz$ ,  $V_o = ?$

$$V_{in} = V_m \sin \omega t = 6 \times 10^{-3} \sin(2\pi f t) = 6 \times 10^{-3} \sin(40000\pi t)$$

Output Voltage,

$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt + V_o(0)$$

$$= -\frac{1}{100 \times 10^3 \times 1 \times 10^{-6}} \int_0^t 6 \times 10^{-3} \sin(40000\pi t) dt$$

Assume  $V_o(0) = 0$

Initial V<sub>o</sub> across capacitor = 0



$$= -10 \left[ (6 \times 10^{-3}) \left( \frac{-\cos(40000\pi t)}{40000\pi} \right)^t \right]$$


$$V_o = 477.46 [\cos(40000\pi t) - 1] \text{ mV}$$

- 26) The input to a Ideal differentiator is a Sinusoidal Voltage of Peak Voltage 6mV & frequency 20 kHz. Find the output Voltage, Given  $R = 100 \text{ K}\Omega$  &  $C = 1 \text{ nF}$ .

sol: Given  $R = 100 \text{ K}\Omega$ ,  $C = 1 \text{ nF}$ ,  $V_m = 6 \text{ mV}$ ,  $f = 20 \text{ kHz}$ .

$$V_{in} = V_m \sin(\omega t) = 6 \times 10^{-3} \sin(40000\pi t)$$

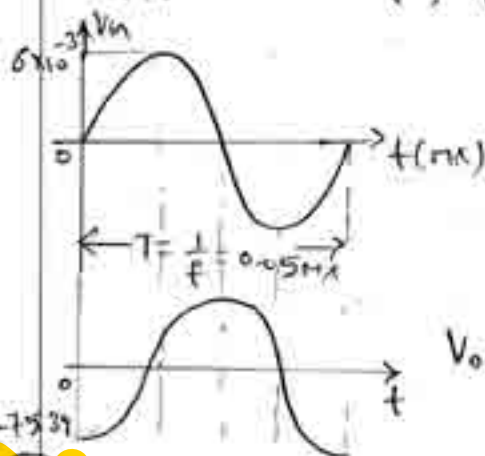Output Voltage,  $V_o = -RC \frac{dV_{in}}{dt}$



$$= -100 \times 10^3 \times 1 \times 10^{-6} \frac{d[6 \times 10^{-3} \sin(40000\pi t)]}{dt}$$

$$= -0.1 \times 6 \times 10^{-3} \cos(40000\pi t) \cdot 40000\pi$$

$$V_o = -75.39 \cos(40000\pi t) \text{ V}$$

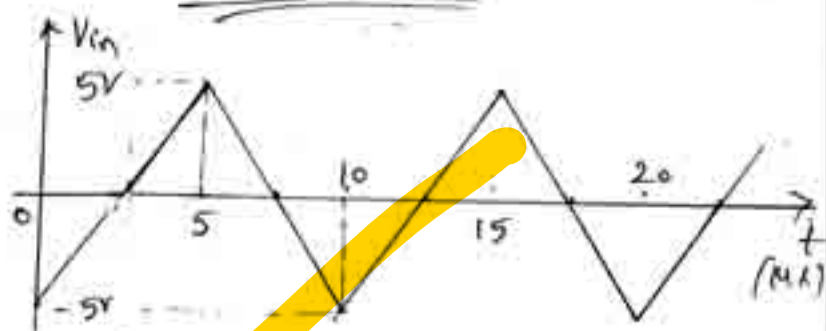


Fig (27)

- 27) Determine the output Voltage of a Ideal differentiator for the input shown in fig (27). Given  $RC = 1 \text{ mV}$ .

sol: Given  $RC = 1 \text{ mV}$

case (1): For  $0 < t < 5 \text{ ms}$

$$\frac{dV_{in}}{dt} = \frac{5 - (-5)}{(5 - 0)} = 2 \text{ V/ms} \quad \text{--- (2)}$$

Points:  $(0, -5)$  and  $(5, 5)$

$$\frac{y_2 - y_1}{x_2 - x_1} = \frac{y - y_1}{x - x_1}$$

$$\Rightarrow y = 2x - 5$$

At  $t = 0$ ,  $V_{in} = 2(0) - 5 = -5 \text{ V}$

Diff. w.r.t  $t$

$$\frac{dV_{in}}{dt} = 2 \text{ V/ms}$$



$$\therefore V_o = -RC \frac{dV_{in}}{dt} = -1 \times 10^6 \frac{2}{10^{-6}} = \underline{\underline{-2V}}$$

Case (ii): For  $5\text{ms} < t < 10\text{ms}$

$$\frac{dV_{in}}{dt} = \frac{-5-5}{(10-5)} = \frac{-10}{5} = -2\text{V/ms} \quad \text{②}$$

$$\therefore V_o = -RC \frac{dV_{in}}{dt} = -1 \times 10^6 \left( -\frac{2}{10^{-6}} \right)$$

$$= \underline{\underline{2V}}$$

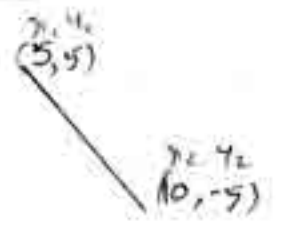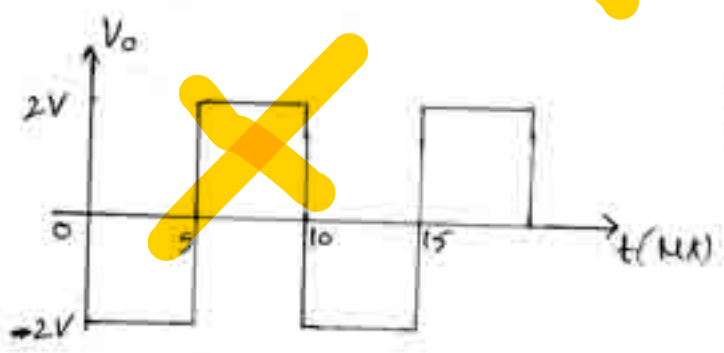

$$\frac{-5-5}{10-5} = \frac{y-5}{x-5}$$

$$\frac{-10}{5} = \frac{y-5}{x-5}$$

$$y-5 = -2x+10$$

$$y = -2x+15$$


$$\frac{dy}{dx} = -2\text{V/ms}$$

28 Calculate

① The output offset voltage due to input offset voltage =  $1.2\text{mV}$

② The output offset voltage due to input offset current =  $100\text{nA}$ .

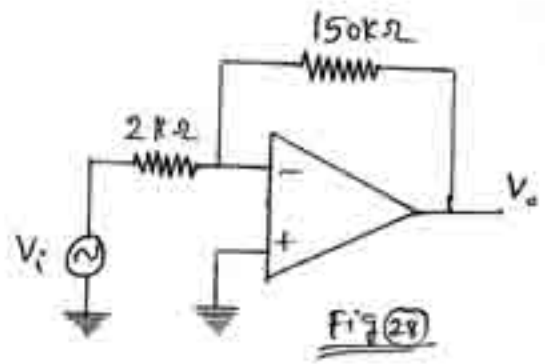③ The output offset voltage due to input offset voltage =  $4\text{mV}$  & input offset current =  $150\text{nA}$ .



Sol:

① Given  $V_{io} = 1.2\text{mV}$

output offset voltage,

$$V_{oo}(\text{due to } V_{io}) = V_{io} \left( \frac{R_i + R_f}{R_i} \right) = 1.2 \times 10^{-3} \left( \frac{2\text{k} + 150\text{k}}{2\text{k}} \right)$$

$$V_{oo}(\text{due to } V_{io}) = \underline{\underline{91.2\text{mV}}}$$



$$\textcircled{b} V_{os}(\text{due to } I_{io}) = I_{io} R_f = 100 \times 10^{-9} \times 150 \times 10^3 = \underline{15 \text{ mV}}$$

$$\textcircled{c} V_{os} = V_{os}(\text{due to } V_{io}) + V_{os}(\text{due to } I_{io})$$

$$= V_{io} \left( 1 + \frac{R_f}{R_i} \right) + I_{io} R_f$$

$$= 4 \times 10^{-3} \left( 1 + \frac{150 \text{ k}}{2 \text{ k}} \right) + 150 \times 10^{-9} (150 \text{ k})$$

$$= 304 \times 10^{-3} + 22.5 \times 10^{-3}$$

$$= \underline{326.5 \text{ mV}}$$

29) Calculate the input bias currents at each input of an op-amp having input bias current =  $30 \text{ nA}$  & Input offset current =  $5 \text{ nA}$

Sol:

$$\text{We have: } I_1 = I_{ib} + \frac{I_{io}}{2} \quad \& \quad I_2 = I_{ib} - \frac{I_{io}}{2}$$

$$= 30 \times 10^{-9} + \frac{5 \times 10^{-9}}{2}$$

$$= \underline{32.5 \text{ nA}}$$

$$= 30 \times 10^{-9} - \frac{5 \times 10^{-9}}{2}$$

$$= \underline{27.5 \text{ nA}}$$

30) For an op-amp having a slew rate of  $2 \text{ V}/\mu\text{s}$ , what is the maximum closed-loop voltage gain that can be used when the input signal varies by  $0.5 \text{ V}$  in  $10 \mu\text{s}$ ?

Sol:

$$\text{We have } V_o = A V_{in}$$


$$\Rightarrow dV_o = A dV_{in}$$

$$\Rightarrow \frac{dV_o}{dt} = A \frac{dV_{in}}{dt}$$

$$\Rightarrow A = \frac{dV_o/dt}{dV_{in}/dt} = \frac{SR}{dV_{in}/dt} = \frac{2/10^{-6}}{0.5/10 \times 10^{-6}} = \underline{40}$$

Maximum closed-loop voltage gain =  $40$ .

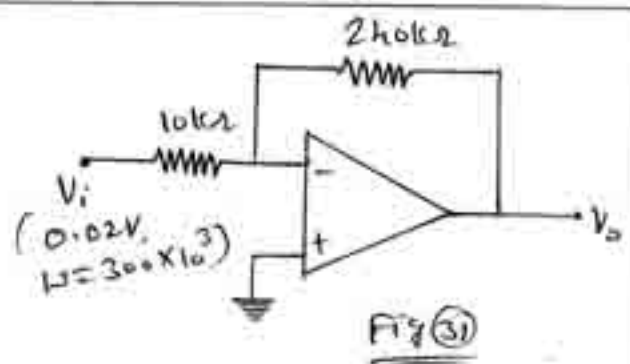31) For the signal & circuit of fig (31), determine the max frequency that may be used. OP-amp Slew rate =  $0.5 \text{ V}/\mu\text{s}$ .



Sol: Gain  $A = \left| \frac{R_f}{R_i} \right| = \frac{240 \times 10^3}{10 \times 10^3} = 24$

Output Voltage (maximum)

$$V_m = A V_i = 24 \times 0.02 = 0.48 \text{ V}$$


We have  $\omega_m \leq \frac{SR}{V_m}$  @  $f_m \leq \frac{SR}{2\pi V_m}$

$$\leq \frac{0.5/10^{-6}}{0.48} \leq \frac{0.5/10^{-6}}{2\pi \times 0.48}$$

$$\omega_m \leq 1.041 \times 10^6 \text{ rad/s} @ f_m \leq 165.78 \text{ kHz}$$

Since the signal's frequency ( $\omega = 300 \times 10^3 \text{ rad/s}$ ) is less than the maximum freq  $\omega_m$ , no output distortion will result.

2) For the circuit shown in fig (32).

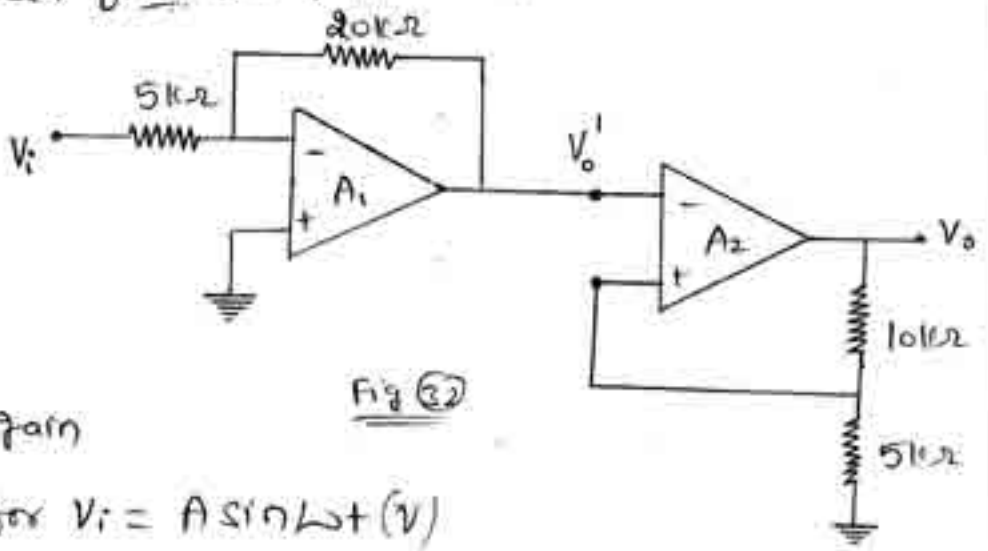

a) Calculate  $A_1$

b) Calculate  $A_2$

c) Find the total gain

d) Find  $V_o'$  &  $V_o$  for  $V_i = A \sin \omega t (\text{V})$

Sol:

a)  $A_1 = -\frac{20\text{k}}{5\text{k}} = -4$     b)  $A_2 = 1 + \frac{10\text{k}}{5\text{k}} = 3$

c)  $A = A_1 A_2 = -12$

$$\textcircled{d} V_0' = (-2) A \sin \omega t = -2A \sin \omega t (V)$$

$$V_0 = A_2 V_0' = 3 (-2A \sin \omega t) = -6A \sin \omega t (V)$$

33) Design an op-amp circuit for  $V_0 = 2V_1 - 3V_2 + 4V_3 - 5V_4$

$$\text{Sol: } V_0 = 2V_1 - 3V_2 + 4V_3 - 5V_4$$

$$\Rightarrow V_0 = (2V_1 + 4V_3) - (3V_2 + 5V_4)$$

$$V_0 = V_{01} - V_{02} \rightarrow \textcircled{1} \text{ where } V_{01} = 2V_1 + 4V_3$$

$$V_{02} = 3V_2 + 5V_4$$

Eqn ① is the expression for output voltage of subtractor.

Consider

$$V_{01} = 2V_1 + 4V_3$$

Comparing with,

$$V_{01} = \frac{R_{f1}}{R_1} V_1 + \frac{R_{f1}}{R_3} V_3$$

$$\Rightarrow \frac{R_{f1}}{R_1} = 2, \quad \frac{R_{f1}}{R_3} = 4$$

$$\text{Let } R_{f1} = 100k\Omega$$

$$\therefore R_1 = 50k\Omega, R_3 = 25k\Omega$$

Consider

$$V_{02} = 3V_2 + 5V_4, \text{ Comparing with}$$

$$V_{02} = \frac{R_{f2}}{R_2} V_2 + \frac{R_{f2}}{R_4} V_4$$

$$\Rightarrow \frac{R_{f2}}{R_2} = 3, \quad \frac{R_{f2}}{R_4} = 5$$

$$\text{Let } R_{f2} = 150k\Omega$$

$$R_2 = 50k\Omega, R_4 = 30k\Omega$$

The op-amp circuit is shown below

$$\text{Let } R = 20k\Omega$$

